

Gm-C Filter – 1

Implementation

Fall 2005
Rev. 0.2



- 1- Introduction to Gm-C Filters
- 2- Filter Implementation Techniques
 - SFG
 - Element replacement
 - Chain Method
- 3- Differential Gm Cells
- 4- Double Input Gm Cells




Introduction: Comparison

3/61

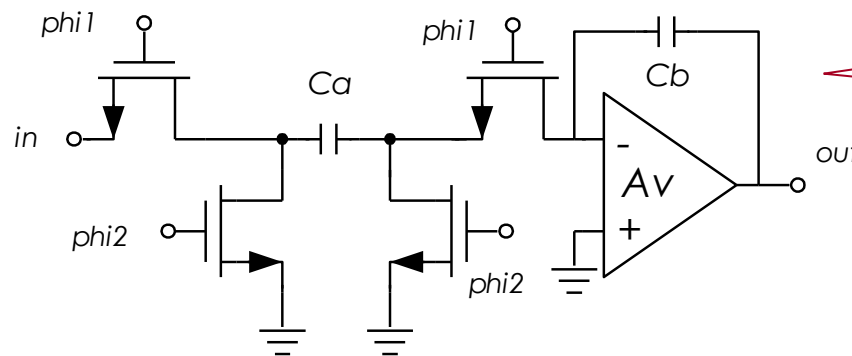Problems with SCF:

- 1- Need to smoothing post filtering
- 2- Need to anti-aliasing pre filtering
- 3- Need to high SR/BW amplifiers
- 4- Clock feed-through problem
- 5- Good for low-freq applications since needs to high frequency clock and hence high power dissipation (>1 MHz)



**A SC based
integrator**




Introduction: Comparison

4/61

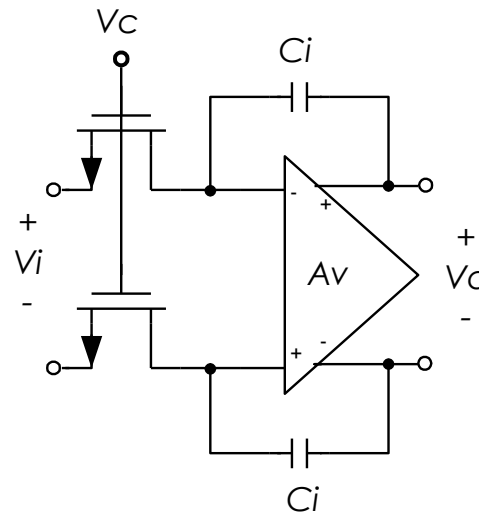Problems with Active-RC/MOSFET-C:

- 1- Need of high SR/BW amplifiers
- 2- Proper for low-freq applications ($>2-3$ MHz)
- 3- Need very high **R** or **C** values with high precision to Implement filters



Introduction: Comparison

General Points for Integrated Filters

- 1- Designer requires deep knowledge on process:
 - $R_{total} < 40 \text{ k}\Omega$ (Accuracy 20%)
 - $C_{total} < 50 \text{ pF}$ (Accuracy 10%)
- 2- Tuning is unavoidable (else than SC filters)
- 3- Implementing very low or very high frequency filters are very difficult
- 4- Single ended configuration results in high non-linearity, distortion, and sensitivity to noise




Overall Specifications of Gm-C Filters:

- 1- Proper for High Freq Applications (~1 MHz and beyond) since there is no feedback
- 2- Uses just Gm Cell Plus Cap to Implement the Filter
- 3- Proper for Medium Accuracy Applications (DR~ 40-60 dB)
- 4- Tunability of filter by Gm variation
- 5- Less area of Gm cell respect to OpAmp

Ideal Gm-C Integrator:
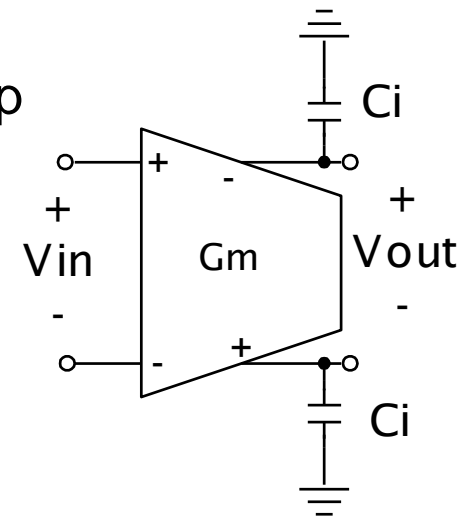
$$\frac{V_o}{V_i} = \frac{G_m}{s \cdot C_i} \quad \omega_0 = \frac{G_m}{C_i}$$




Overall Specifications of Gm-C Filters:

- 6-Gm cell must be linear for whole voltage swing (there is no feedback and no virtual ground)
- 7- Needs to high output impedance




Introduction: Gm Cell

Gm symbol

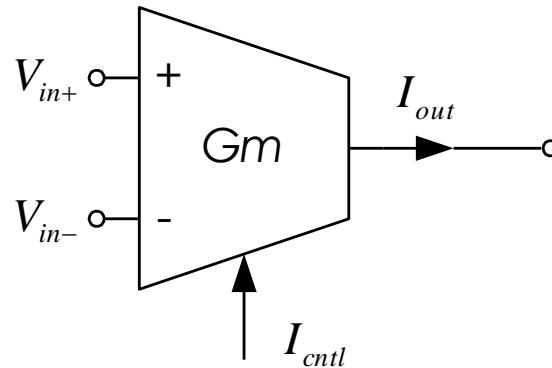


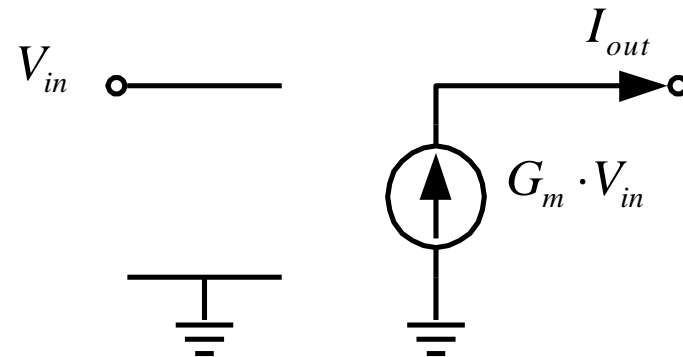Ideal Gm Model: output current is proportional to the input voltage



Introduction: Gm Cell

Symmetric Gm cell:


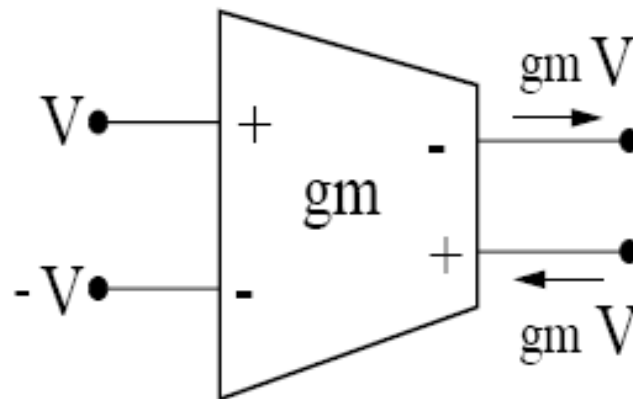


$$I_{out} = I_{plus} - I_{minus} = g_m(V_{plus} - V_{minus}) = g_m V_{in}$$




Introduction: Gm Cell

Practical Gm Model

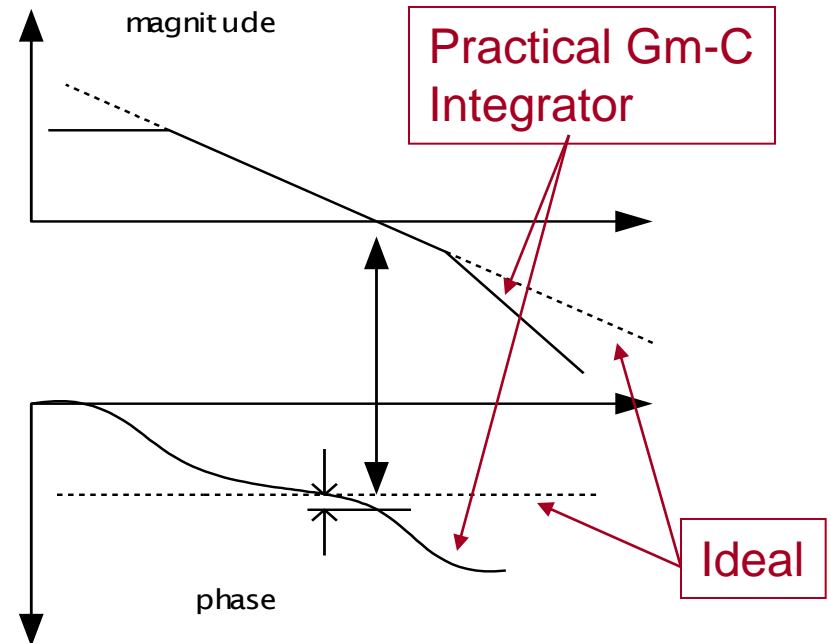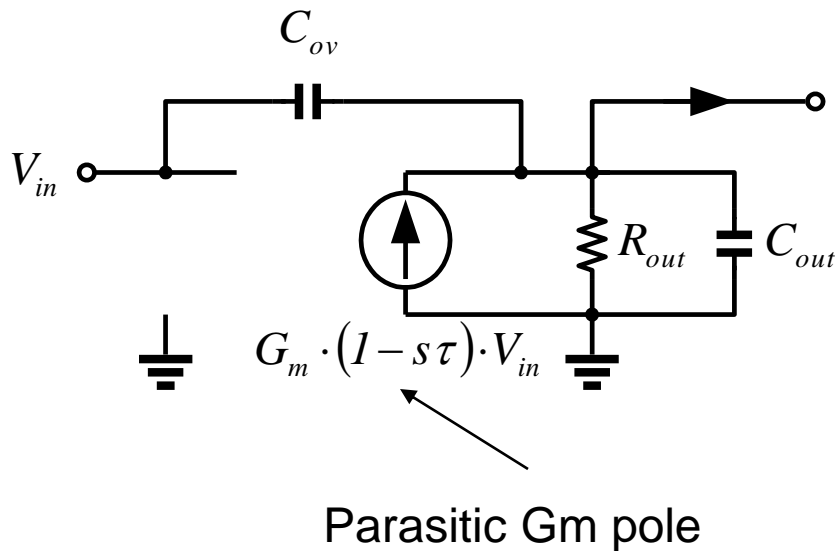

Introduction: Gm Cell


Practical integrator

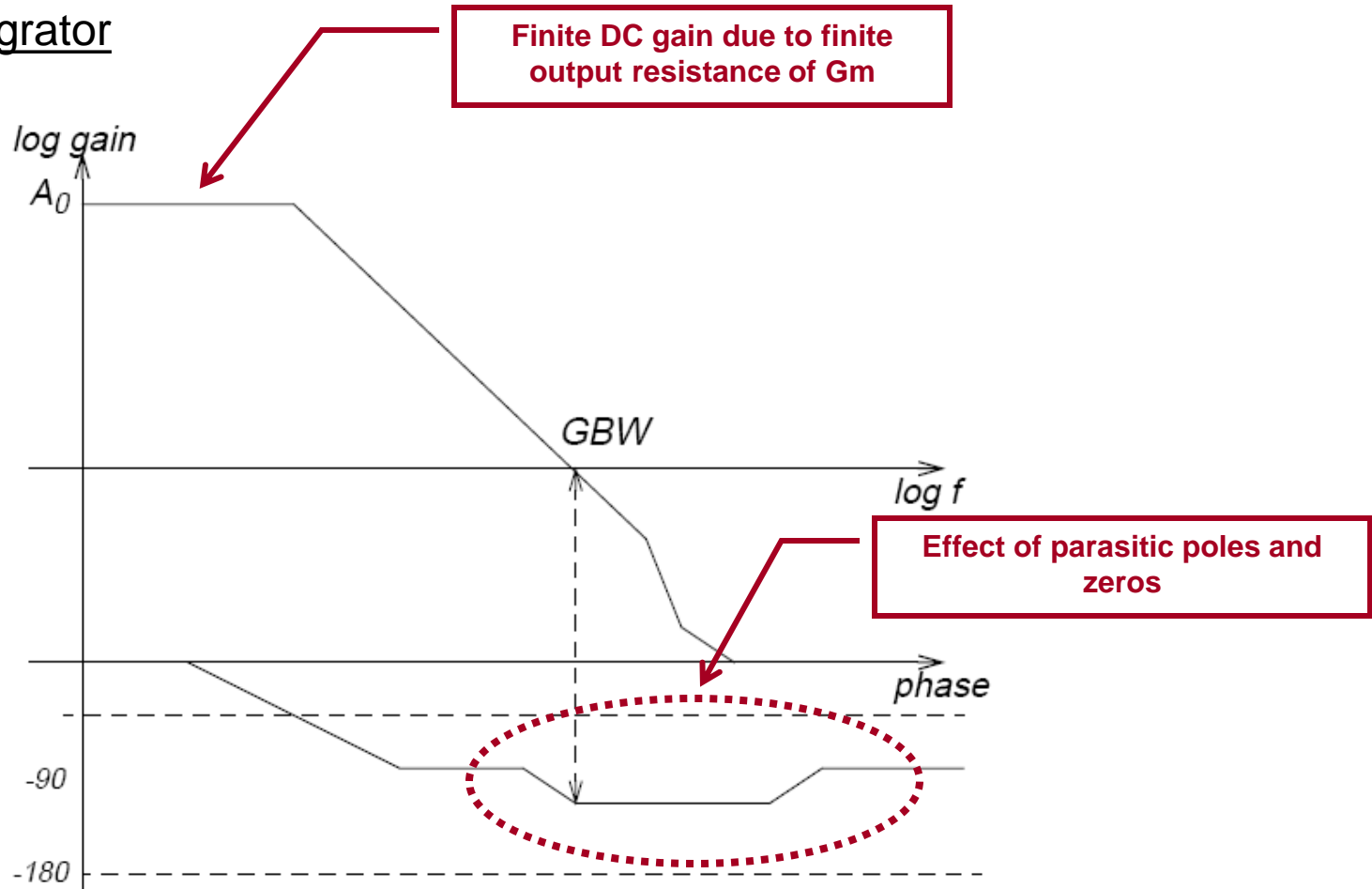

Gm Cell VS OPAMP

Opamp


Voltage controlled
voltage source

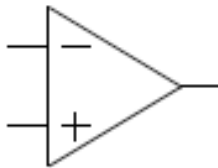

- Low output impedance
- Output in the form of voltage
- Can drive R-loads
- Good for RC filters, OK for SC filters
- Extra buffer adds complexity, power dissipation

OTA

Voltage controlled
current source

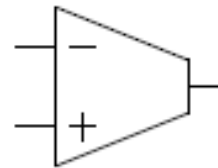

- High output impedance
- In the context of filter design called gm-cells
- Output in the form of current
- Cannot drive R-loads
- Good for SC & gm-C filters
- Typically, less complex compared to opamp → higher freq. potential
- Typically lower power
- no need to complex output stages

Implementation Techniques:

- 1- Element Substitution Technique
- 2- Signal Flow Graph Technique
- 3- Chain Method (Biquad)




Filter Implementation: Replacement Technique

14/61

Replacement Technique:

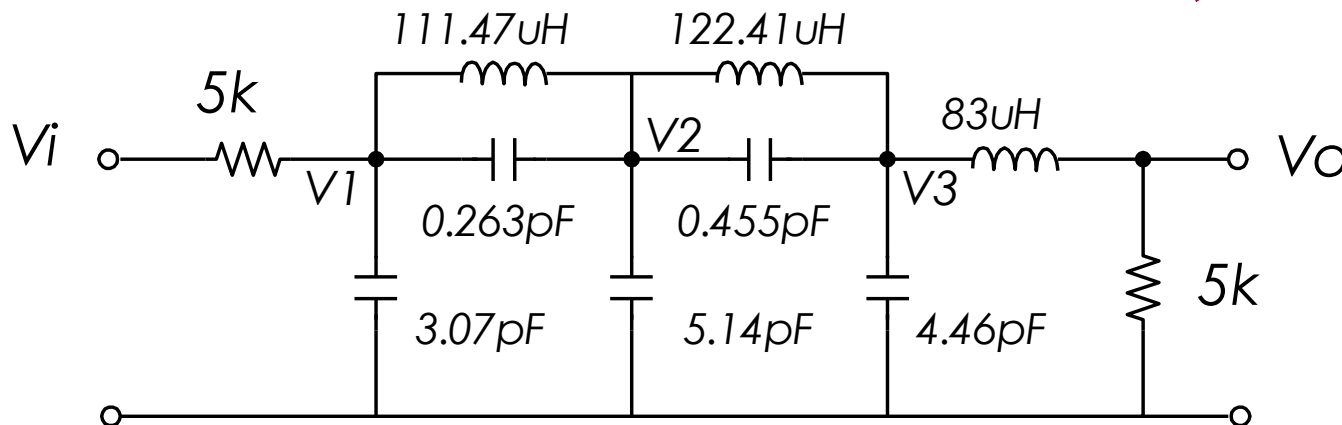Replace **Inductors/Resistors** with Equivalent **Gm-C Gyrator/Transconductor**



Large inductors and capacitors
So, could not be implemented on chip


Example



Filter Implementation: Replacement Technique

15/61

Simulating the grounded R:

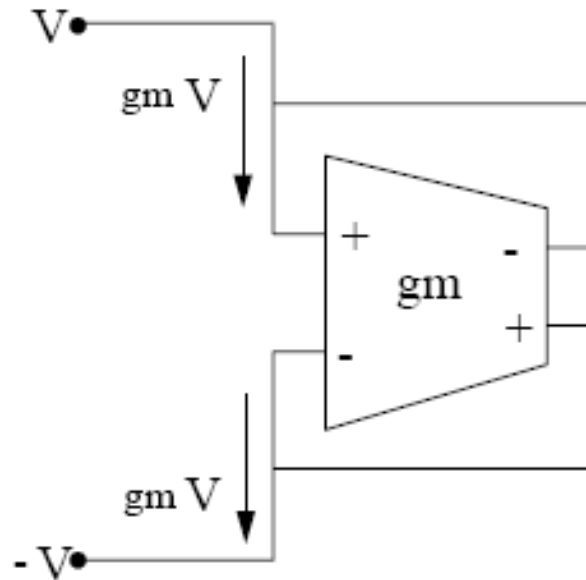


$$R = \frac{V}{I} = \frac{V}{g_m V} = \frac{1}{g_m}$$



Simulating the grounded L:

Active inductor = gyrator

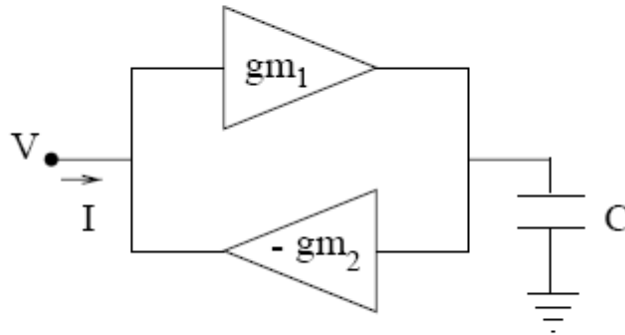

$$L = \frac{C}{g_{m1}g_{m2}}$$


$$Z = \frac{V}{I} = \frac{sC}{g_{m1}g_{m2}}$$



Filter Implementation: Replacement Technique

17/61

Simulating the floating L:

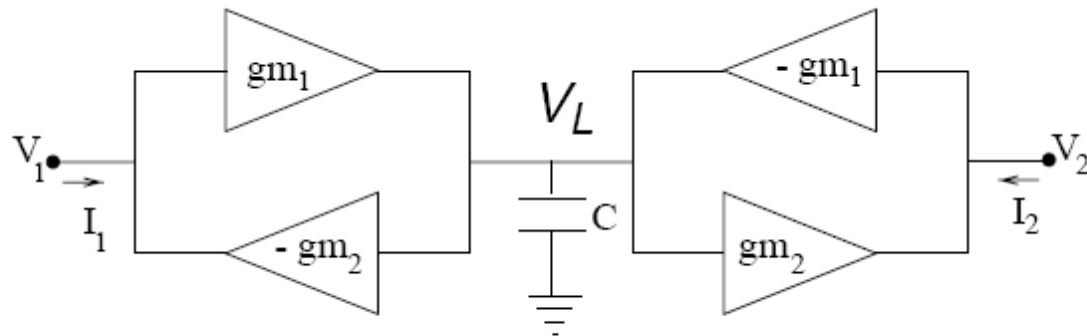

$$sC_L V_L + g_{m1} V_1 - g_{m1} V_2 = 0 \quad V_L = \frac{g_{m1}(V_2 - V_1)}{sC_L}$$


$$I_1 = -g_{m2} \frac{g_{m1}(V_2 - V_1)}{sC_L} \quad I_2 = g_{m2} \frac{g_{m1}(V_2 - V_1)}{sC_L}$$

$$L = \frac{V}{I} = \frac{C_L}{g_{m1}g_{m2}}$$



Filter Implementation: Replacement Technique

Simulating symmetrical floating gyrator:

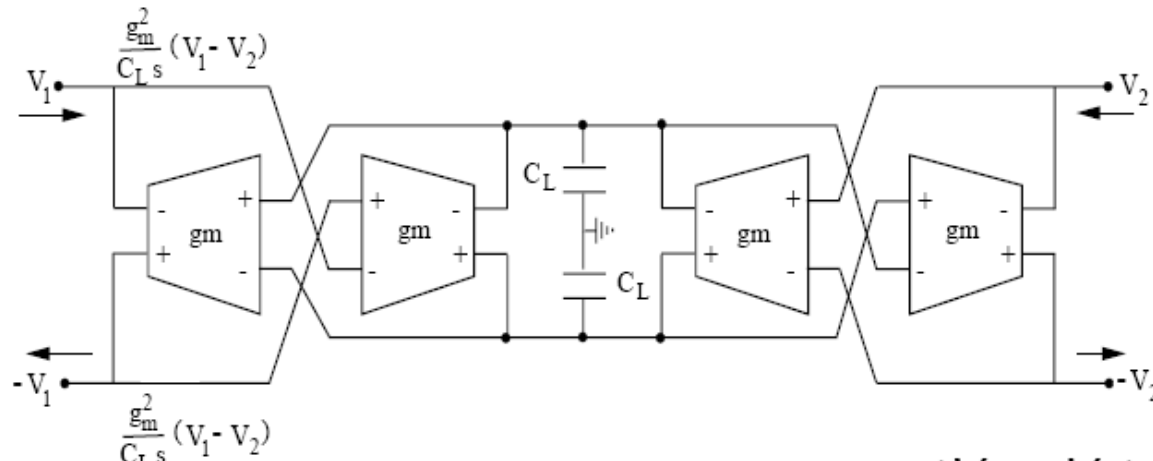

$$sC_L V_L - g_m V_1 + g_m V_2 = 0 \quad V_L = \frac{g_m (V_2 - V_1)}{sC_L}$$





$$I_1 = \frac{g_m^2 (V_1 - V_2)}{sC_L} \quad I_2 = \frac{g_m^2 (V_2 - V_1)}{sC_L}$$

$$L = \frac{V}{I} = \frac{C_L}{g_m^2}$$



Filter Implementation: Replacement Technique


Simulating the passive devices:

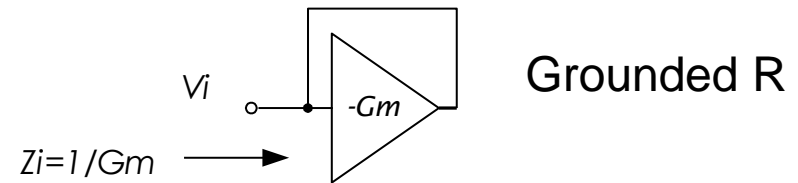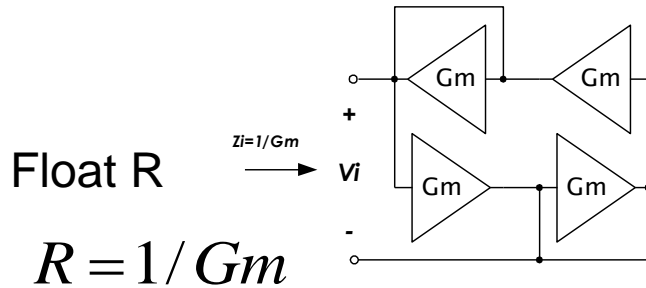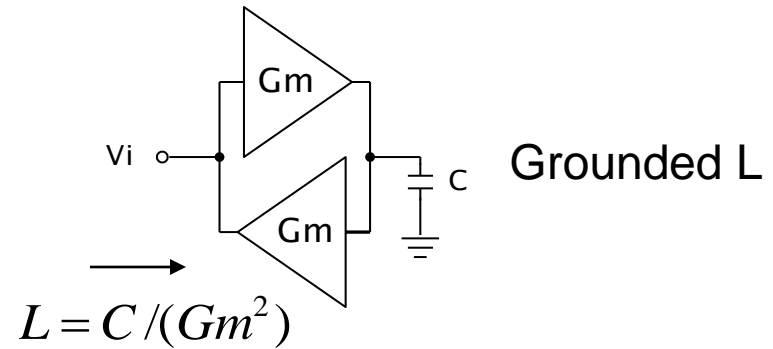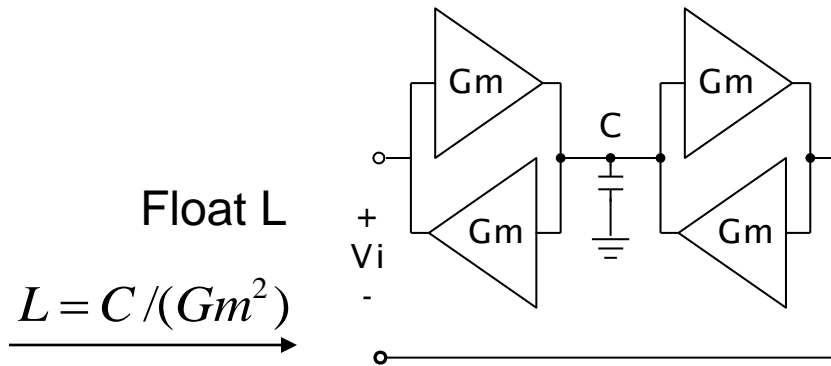


Filter Implementation: Replacement Technique

20/61

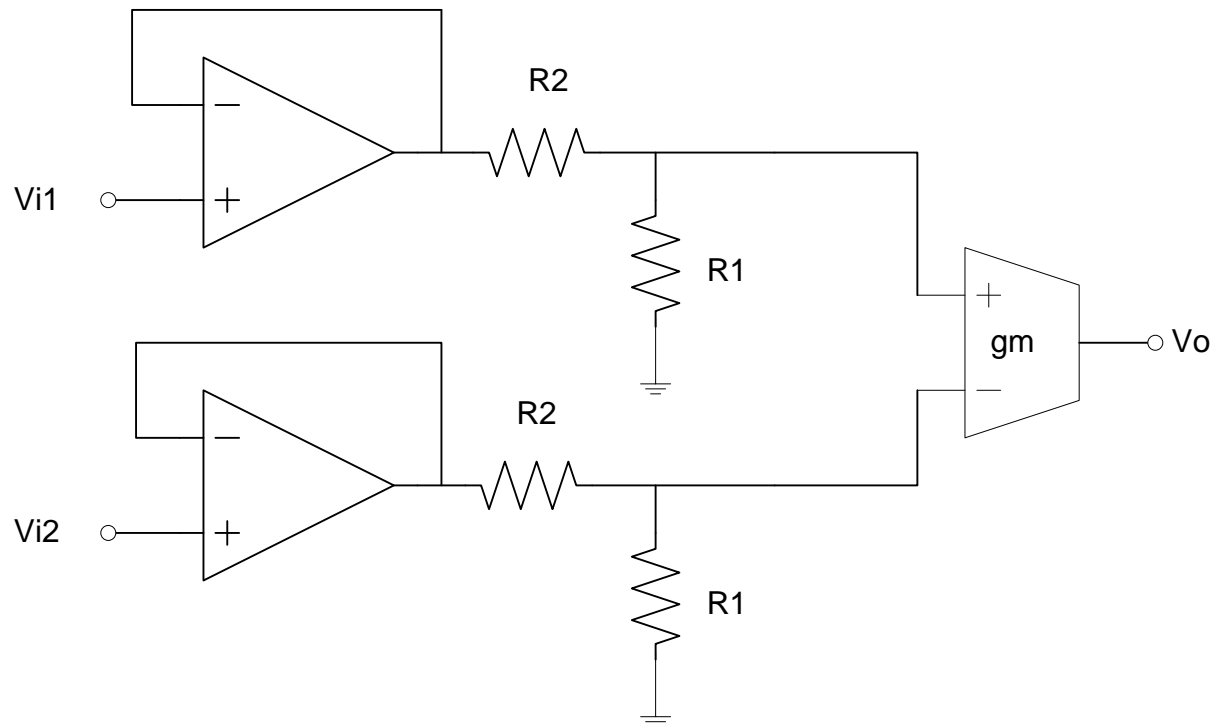Example:
Implementing adder with desired weighting



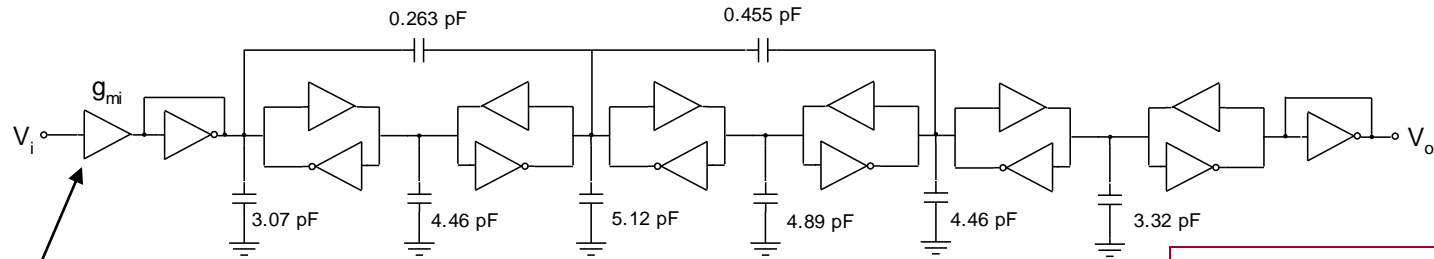
Filter Implementation: Replacement Technique



All $G_m=200 \mu\text{mho}$


$$G_{mi} = 2 \cdot G_m$$

To Eliminate the Input 6-dB Attenuation

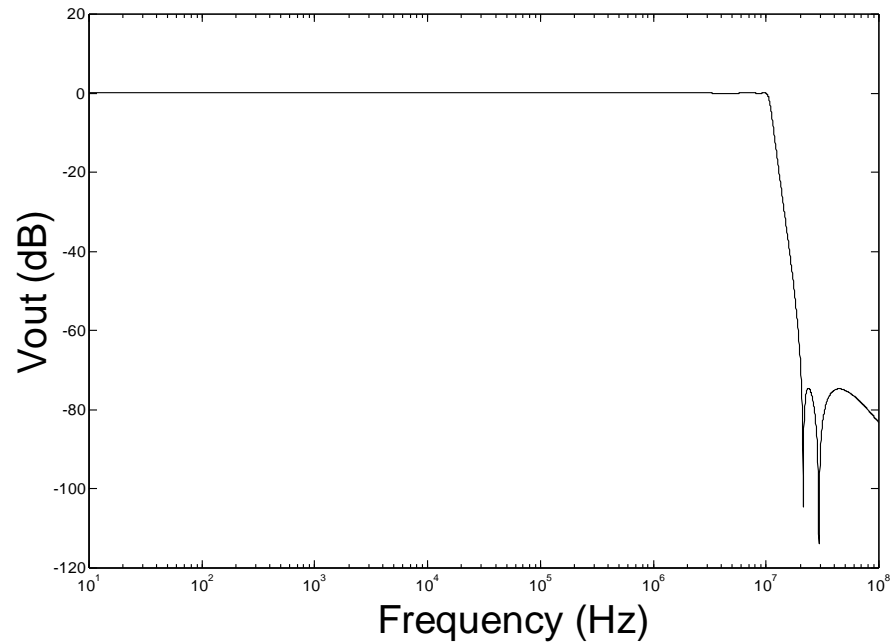


Filter Implementation: Replacement Technique

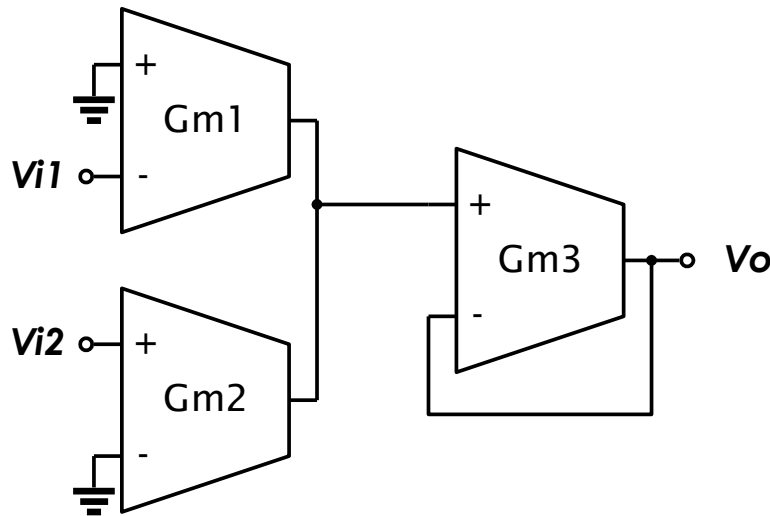Some Other Useful Building Blocks For Replacement


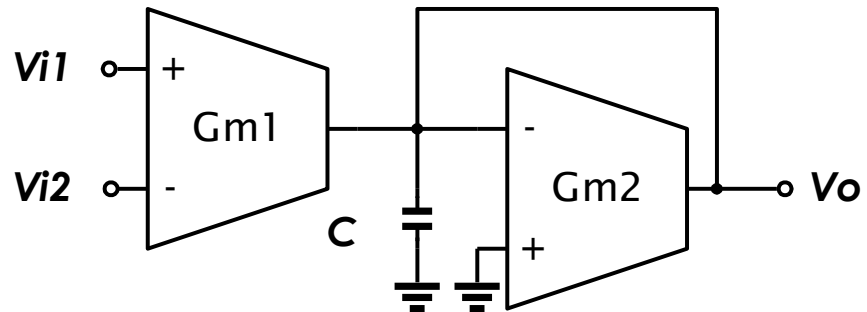
$$V_o = \frac{1}{G_{m3}} \times (-G_{m1} \times V_{i1} + G_{m2} \times V_{i2})$$



$$V_o = \frac{G_{m1}}{sC + G_{m2}} \times (V_{i1} - V_{i2})$$

Lossy integrator

IMPORTANT NOTE:


Adding/subtracting of currents
Is much simpler than voltage
and hence could be helpful to
Design high speed circuits

: Addition and division



Specifications:

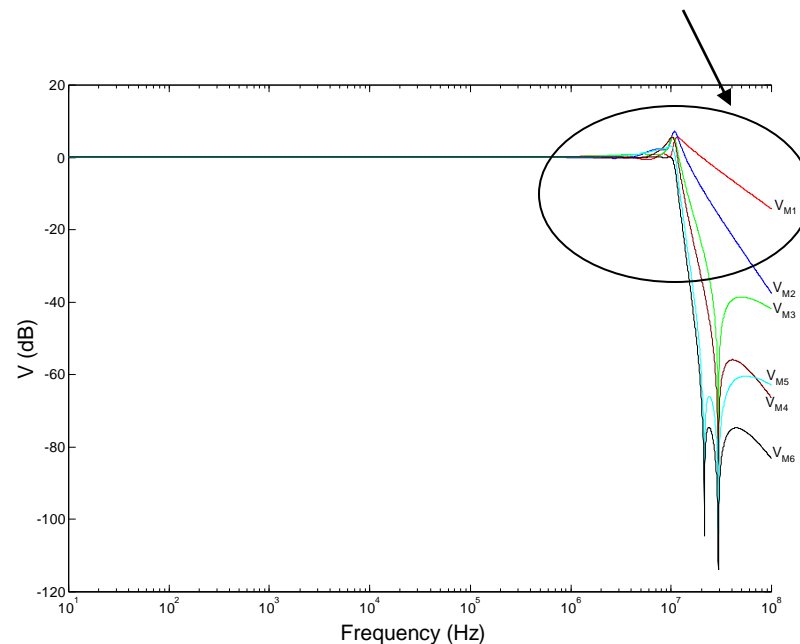- 1- Low sensitivity to device variations, since it is based on LC ladder topology
- 2- There is no general way for optimizing the DR (See the gain of intern=mediate nodes)
- 3- Hard to be tuned (difficult for tuning)



General Specifications of SFG method:

- 1- Low sensitivity to device variations
- 2- Filter implemented based on a LC ladder filter and using basic current/voltage equations in the filter
- 3- To convert finally all currents to voltage, a resistive coefficient of “R” will be used.
- 4- It is possible to optimize the DR (although it could be so much complex)
- 5- Number of transconductors is high



Filter Implementation: SFG

Method:

This method is based on common SFG method in filter implementation
And uses V/I equations to synthesis the filter:

- 0) Using approximations to extract filter transfer function
for example: Chebysheve, Butterworth, and so on.
- 1) Write the basic V/I equations
- 2) Select a nominal R^* to convert all currents to voltages
- 3) Implement them based on active integrator (inverting or non-inverting) building blocks
- 4) Replacing active integrators by Gm-C counterparts
- 5) DR optimization


- It is preferred to use identical Gm cells for better matching and more simple tuning



Filter Implementation: SFG (Step-by-Step)

26/61

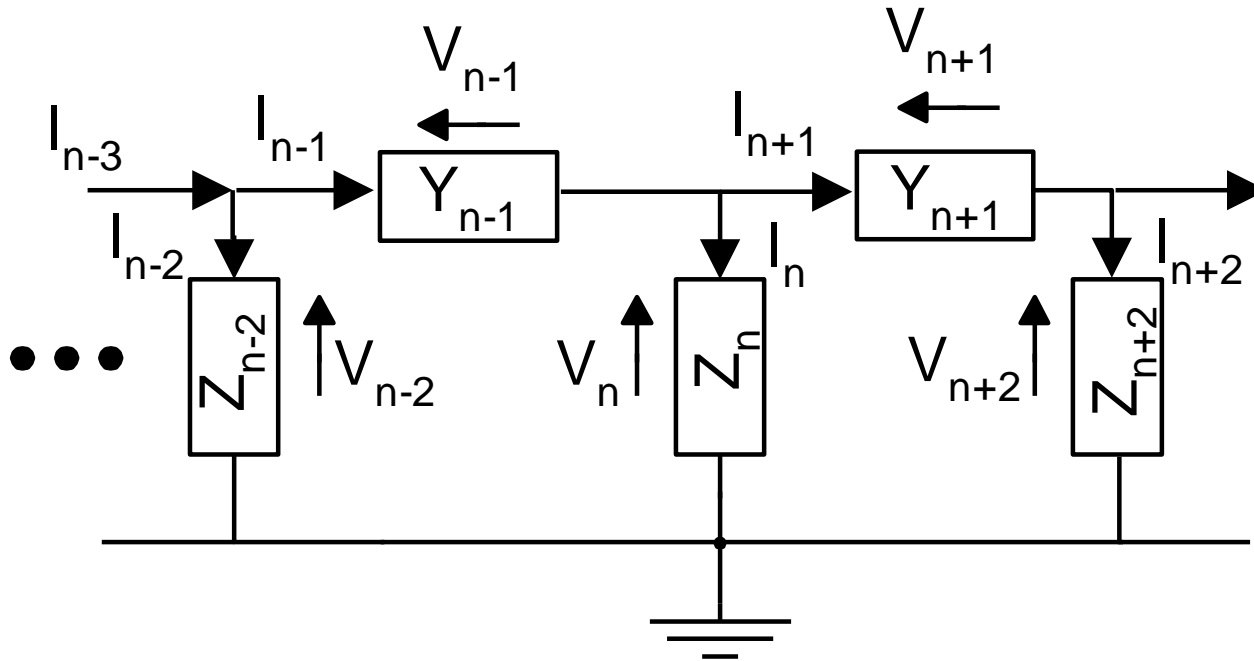- Step 1) Writing the basic equations
- Step 2) Converting all currents to voltages



Filter Implementation: SFG

$$I_{n-2} = I_{n-3} - I_{n-1} \quad V_{n-2} = Z_{n-2} I_{n-2} = Z_{n-2} (I_{n-3} - I_{n-1})$$

$$V_{n-1} = V_{n-2} - V_n \quad I_{n-1} = Y_{n-1} V_{n-1} = Y_{n-1} (V_{n-2} - V_n)$$

$$I_n = I_{n-1} - I_{n+1} \quad V_n = Z_n I_n = Z_n (I_{n-1} - I_{n+1})$$


$$V_{n+1} = V_n - V_{n+2} \quad I_{n+1} = Y_{n+1} V_{n+1} = Y_{n+1} (V_n - V_{n+2})$$

$$I_{n+2} = I_{n+1} - I_{n+3} \quad V_{n+2} = Z_{n+2} I_{n+2} = Z_{n+2} (I_{n+1} - I_{n+3})$$



Filter Implementation: SFG


Implementing based on V/I equations:

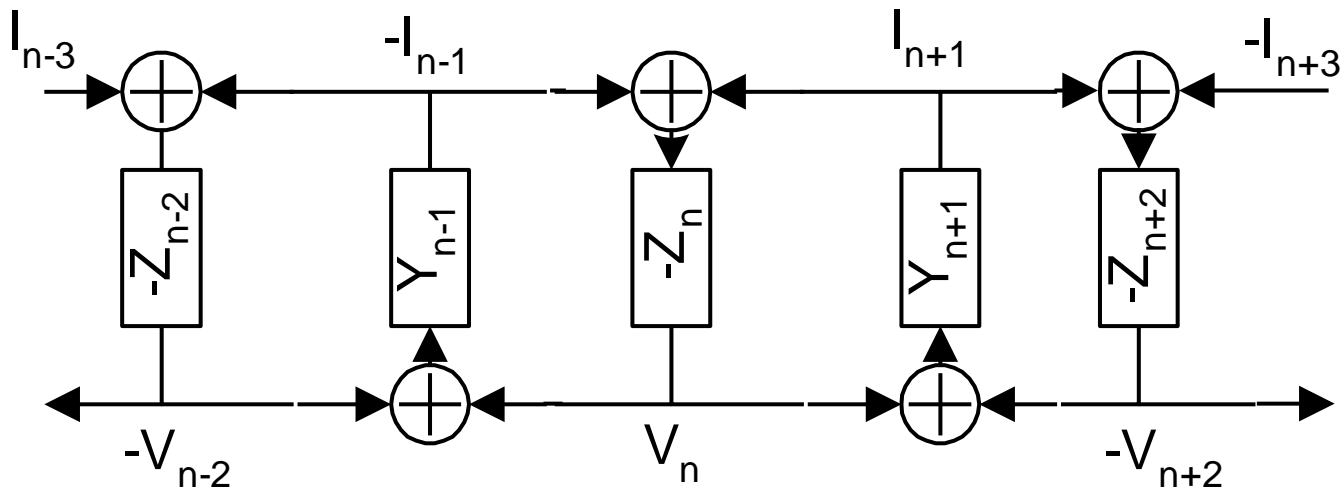

Filter Implementation: SFG

29/61

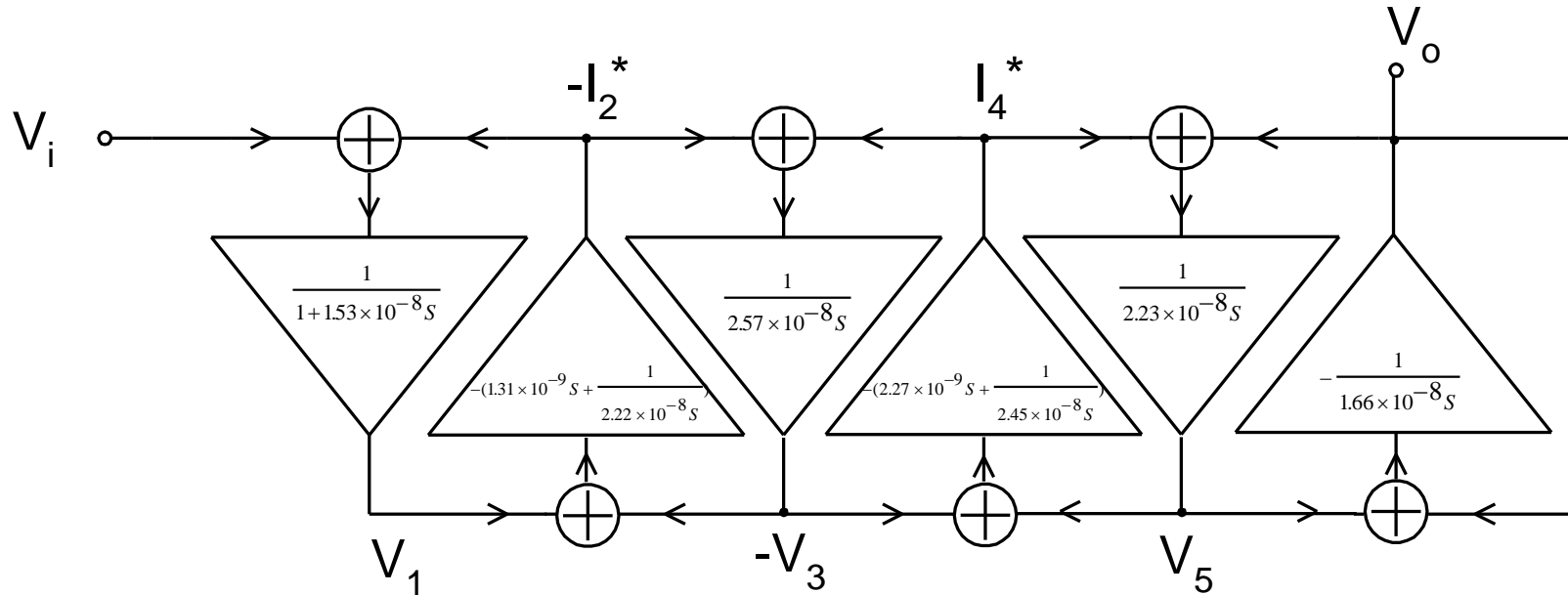
Step 3) Implementation based on active integrators




Filter Implementation: SFG

Step 4) Replacing by Gm-C integrators

Add/filter (second order)

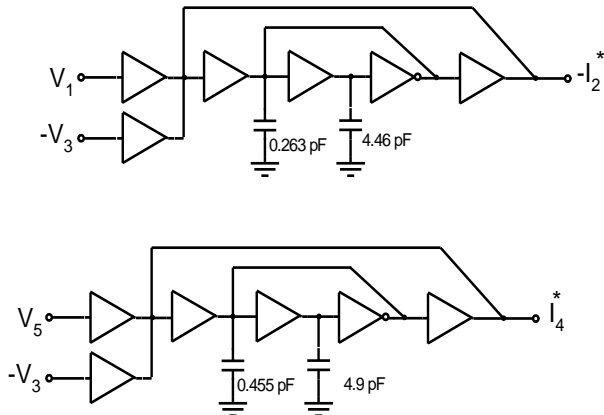


Add/Integrate (lossy)

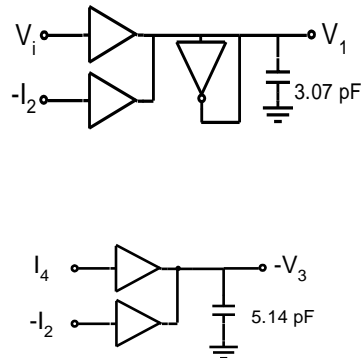

Add/Integrate

Add/Integrate

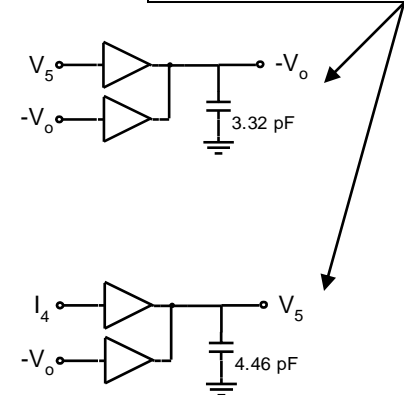


Implementing the Basic Building Blocks Required in SFG Process



Filter Implementation: SFG



Step 5) DR Optimization

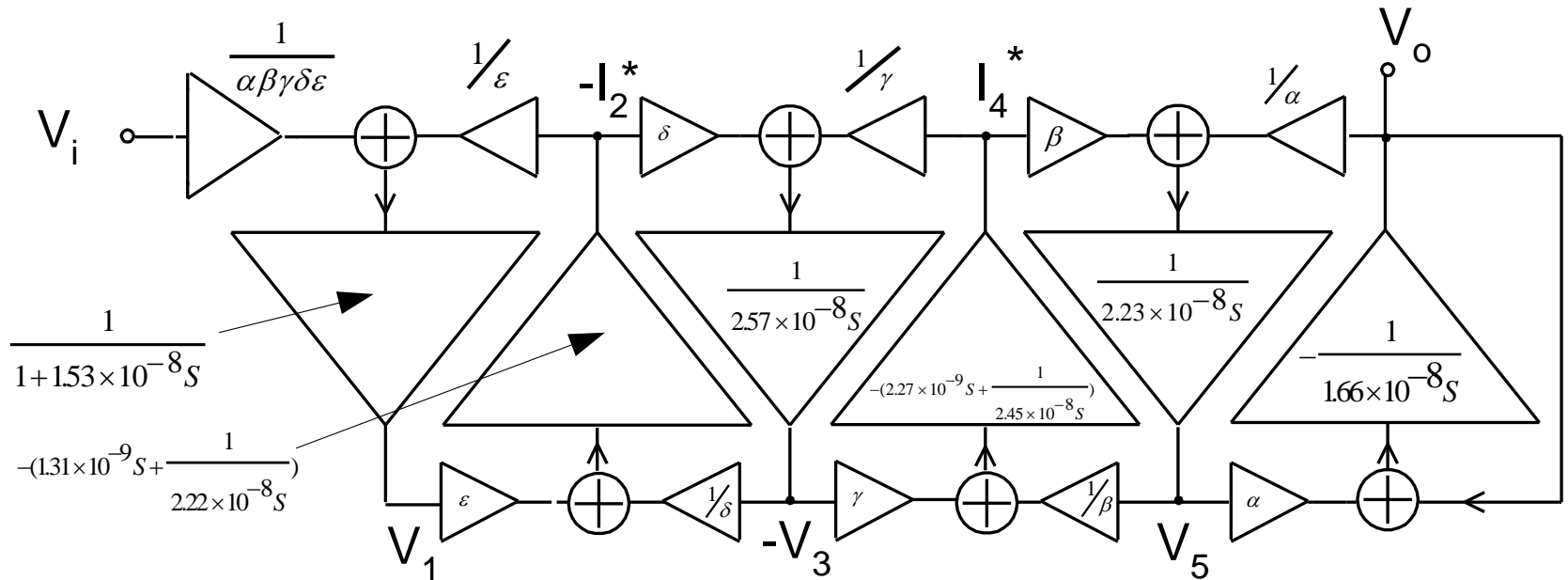

Filter Implementation: SFG

32/61

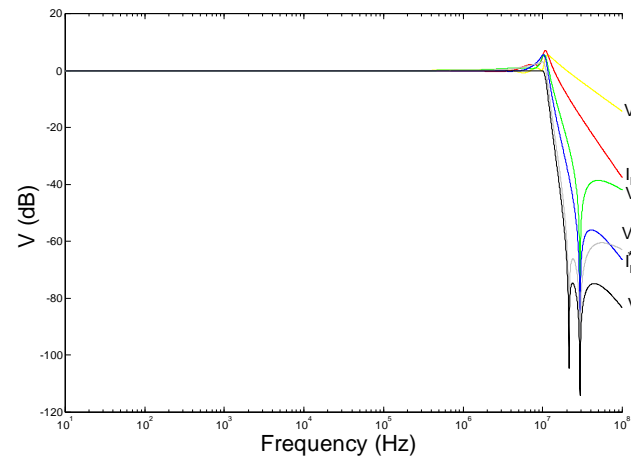
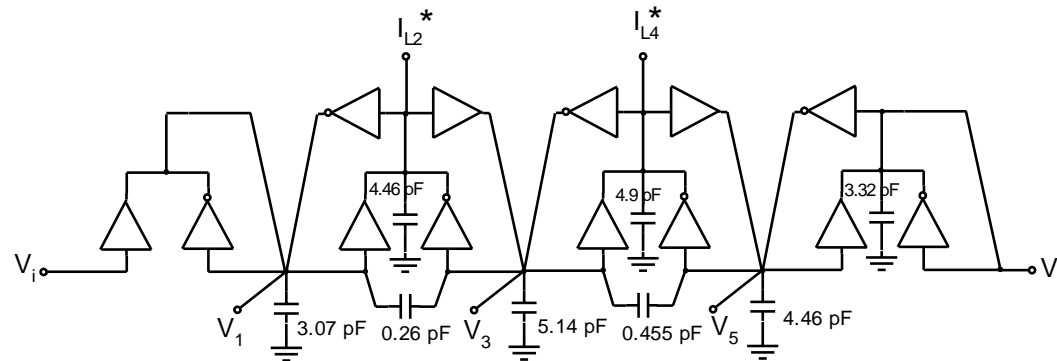
Final Implemented Filter (without DR optimization)



Filter Implementation: SFG

Final Implemented Filter (with optimized DR)

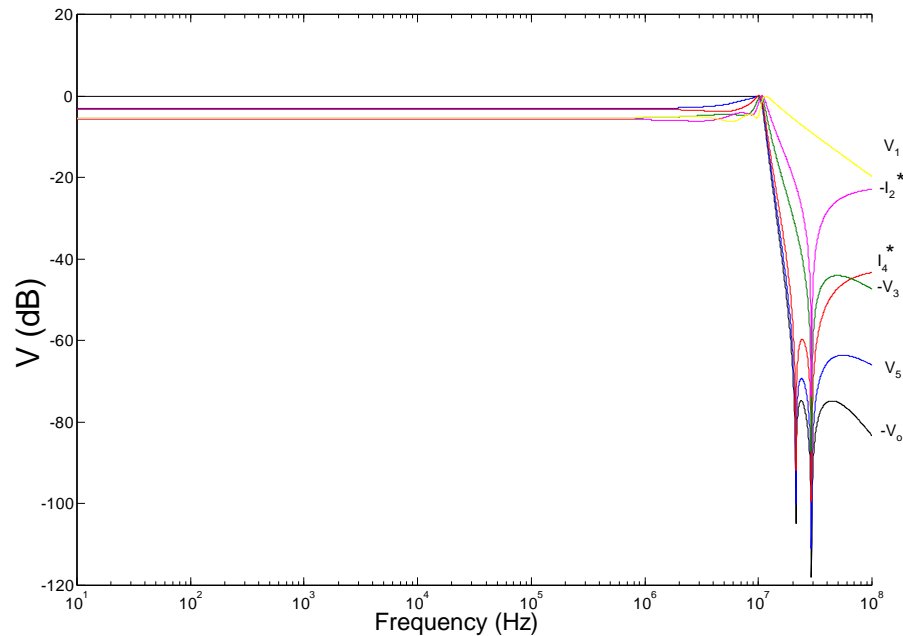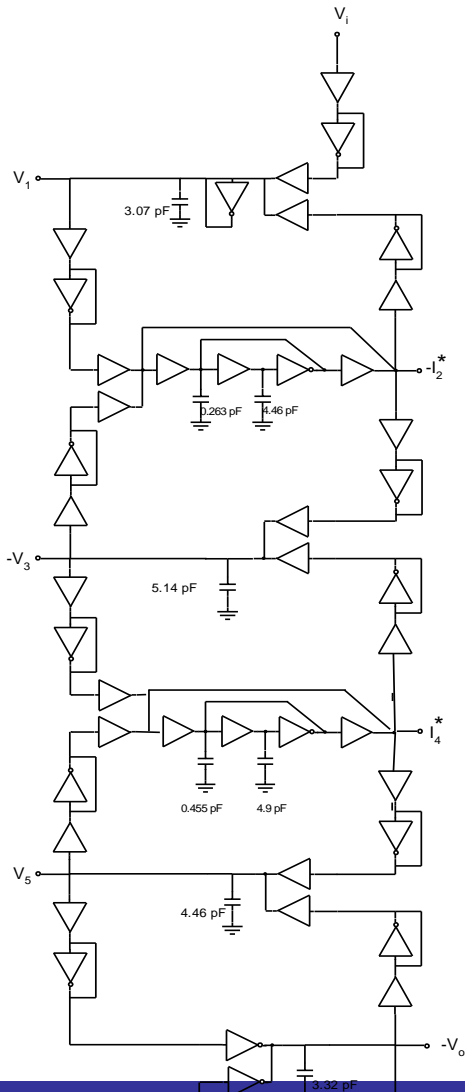← As can be seen, DR optimization need several extra Gm cells



Filter Implementation: SFG

34/61

Example 2: Implementing this filter


Step one :

Equation of voltage of Caps and current of Inductors.

$$V_1 = \frac{1}{C_1} \int \left(\frac{V_i - V_1}{R} - i_2 \right) \cdot dt$$

$$i_2 = \frac{1}{L_2} \int (V_1 - V_o) \cdot dt$$
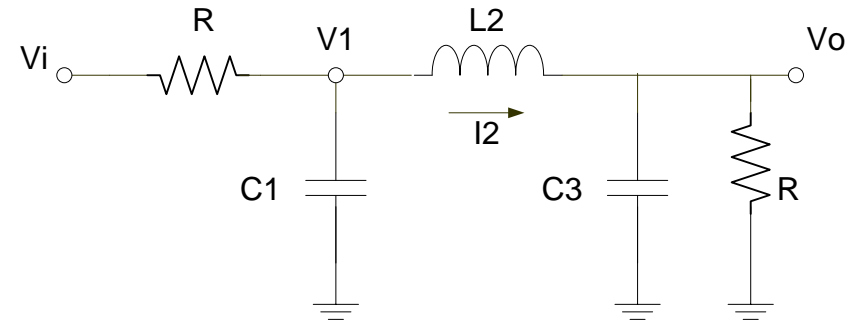
$$V_o = \frac{1}{C_3} \int \left(i_2 - \frac{V_o}{R} \right) \cdot dt$$



Step two :

Convert voltages to currents

$$i^* \rightarrow R^* \cdot i$$


$$R^* = R$$



Filter Implementation: SFG

35/61

Example 2: Implementing this filter

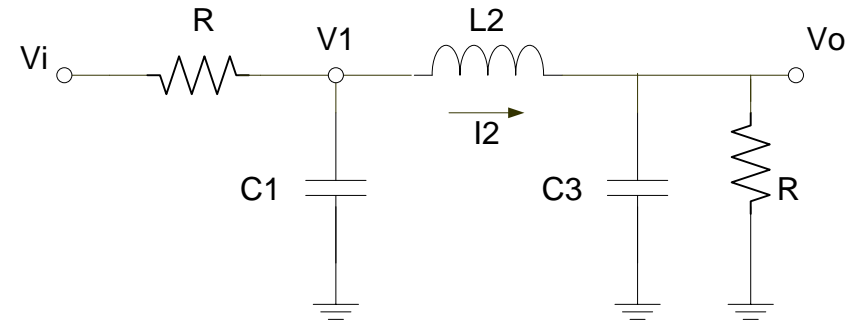

$$V_1 = \frac{1}{C_1} \int \left(\frac{V_i - V_1}{R} - i_2 \right) \cdot dt$$

$$i_2 = \frac{1}{L_2} \int (V_1 - V_o) \cdot dt$$

$$V_o = \frac{1}{C_3} \int \left(i_2 - \frac{V_o}{R} \right) \cdot dt$$



$$\begin{cases} V_1 = \frac{1}{R \cdot C_1} \int ((V_i - V_1) - i_2^*) \cdot dt \\ i_2^* = \frac{R}{L_2} \int (V_1 - V_o) \cdot dt \\ V_o = \frac{1}{R \cdot C_3} \int (i_2^* - V_o) \cdot dt \end{cases}$$




Filter Implementation: SFG

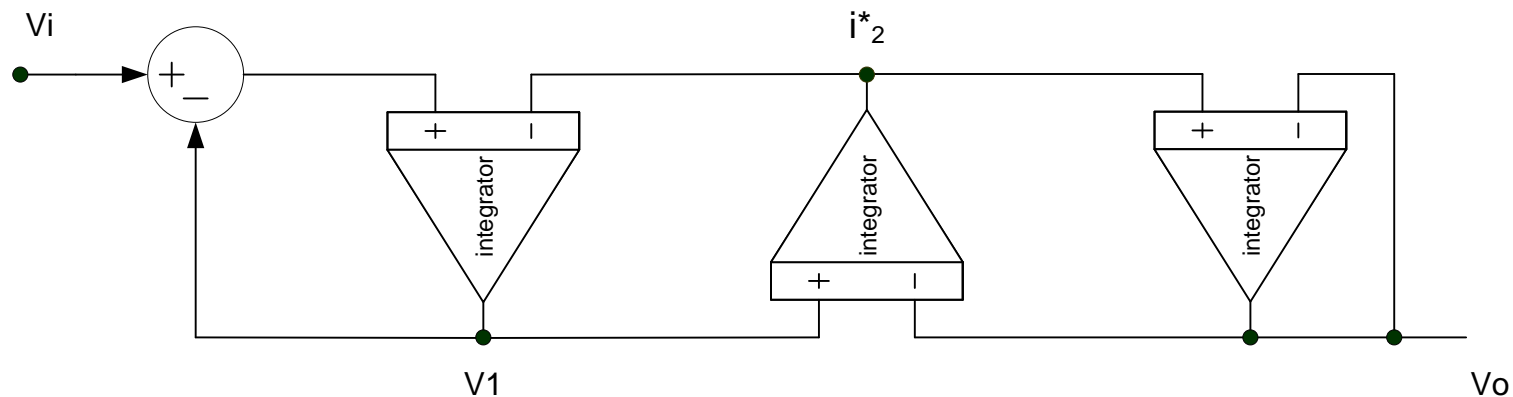Example 2: Implementing this filter

Step three :

Implementation of above equations by using integrators in equivalent circuit




Filter Implementation: SFG

37/61

Step four :

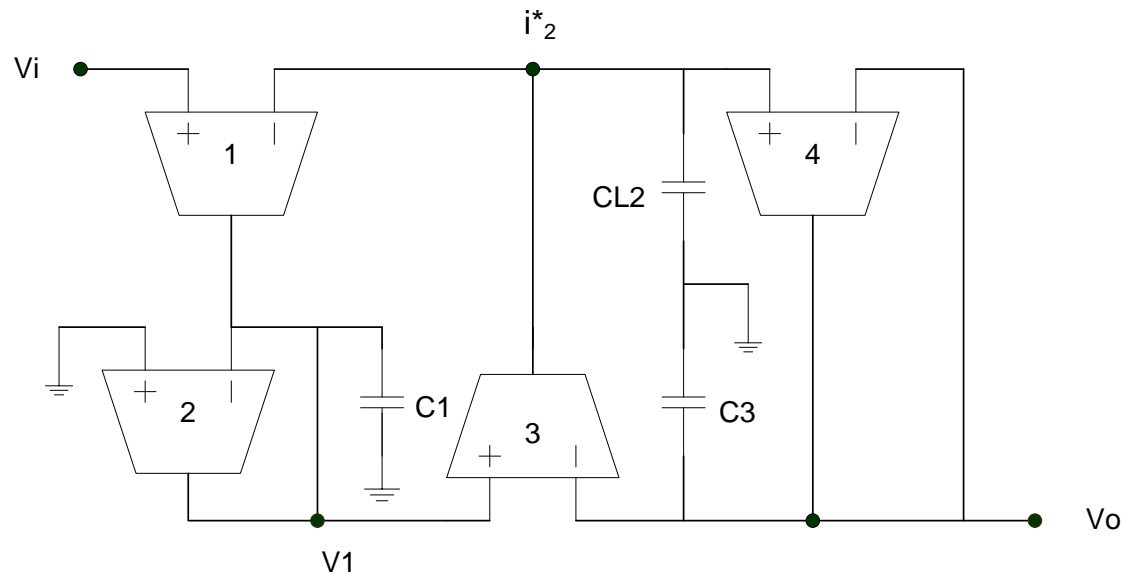Implementation of above circuit by using Gm-C integrators and adders.




Where : $gm_1=gm_2=gm_3=gm_4=gm=1/R$, $CL_2=L_2.gm^2$



Filter Implementation: SFG


38/61

Implementing transmission zeros :

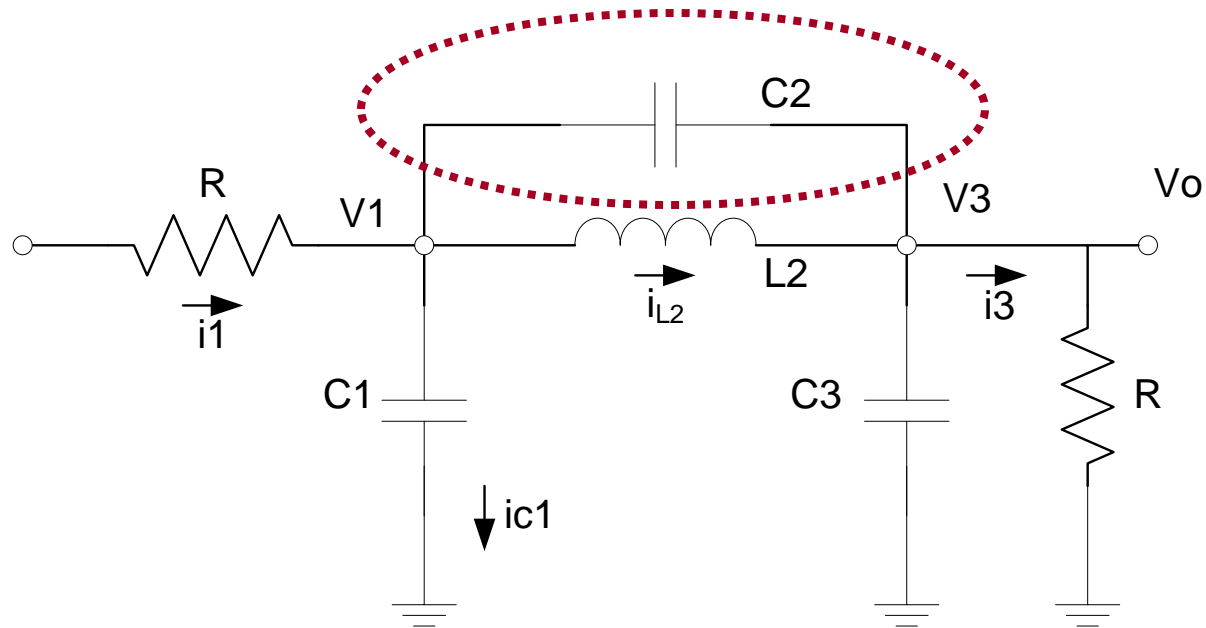

Filter Implementation: SFG

Implementing transmission zeros :

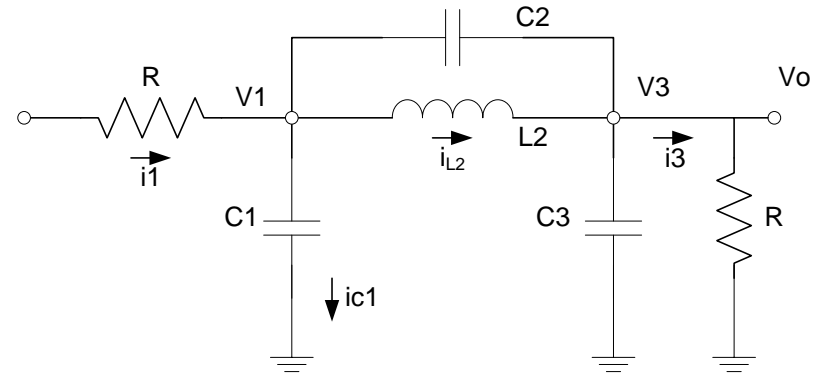

$$I_1 = \frac{V_i - V_1}{R}$$

$$V_1 = \frac{1}{S \cdot C_1} [I_1 - I_{L2} - S \cdot C_2 (V_1 - V_3)]$$

$$I_{L2} = \frac{1}{S \cdot L_2} (V_1 - V_3)$$

$$V_3 = \frac{1}{S \cdot C_3} [I_{L2} - I_3 - S \cdot C_2 (V_3 - V_1)]$$

$$I_3 = \frac{V_3}{R}$$


$$\begin{aligned} I_i^* &\rightarrow R^* \cdot I_i \\ R^* &= R \\ &\rightarrow \rightarrow \end{aligned}$$

$$\left\{ \begin{aligned} I_1^* &= V_i - V_1 \\ V_1 &= \frac{1}{S \cdot C_1 \cdot R} [I_1^* - I_{L2}^* - S \cdot C_2 (V_1 - V_3)] \\ I_{L2}^* &= \frac{R}{S \cdot L_2} (V_1 - V_3) \\ V_3 &= \frac{1}{S \cdot C_3 \cdot R} [I_{L2}^* - I_3^* - S \cdot C_2 \cdot R (V_3 - V_1)] \\ I_3^* &= V_3 \end{aligned} \right.$$




Filter Implementation: SFG

Implementing transmission zeros :

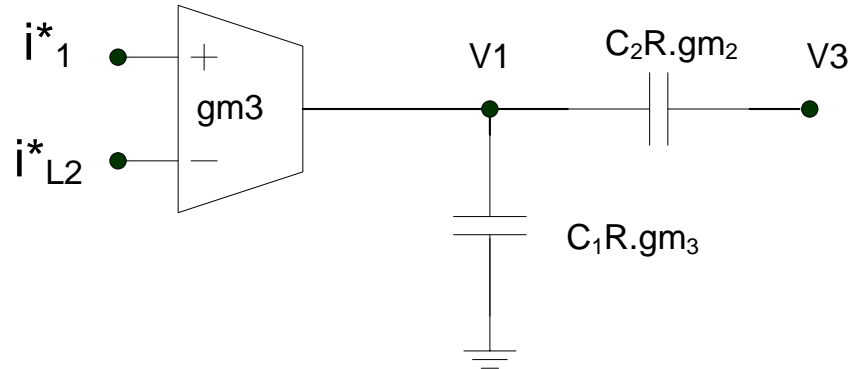
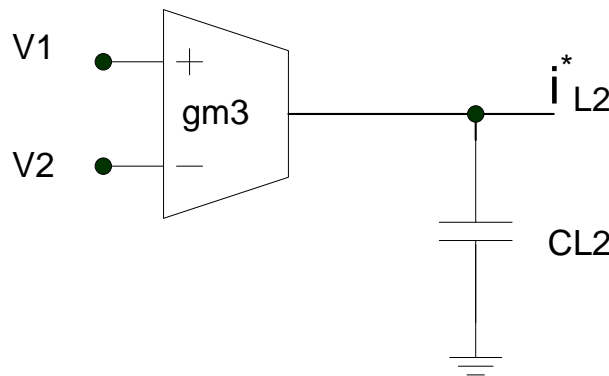
$$gm_3 (I_1^* - I_{L2}^*) = S(C_1 \cdot R \cdot gm_3) V_1 + S(C_2 \cdot R \cdot gm_3) (V_1 - V_3)$$




$$C_{L2} = \frac{L_2 \cdot gm_4}{R}$$



Filter Implementation: SFG



41/61

Implementing transmission zeros :

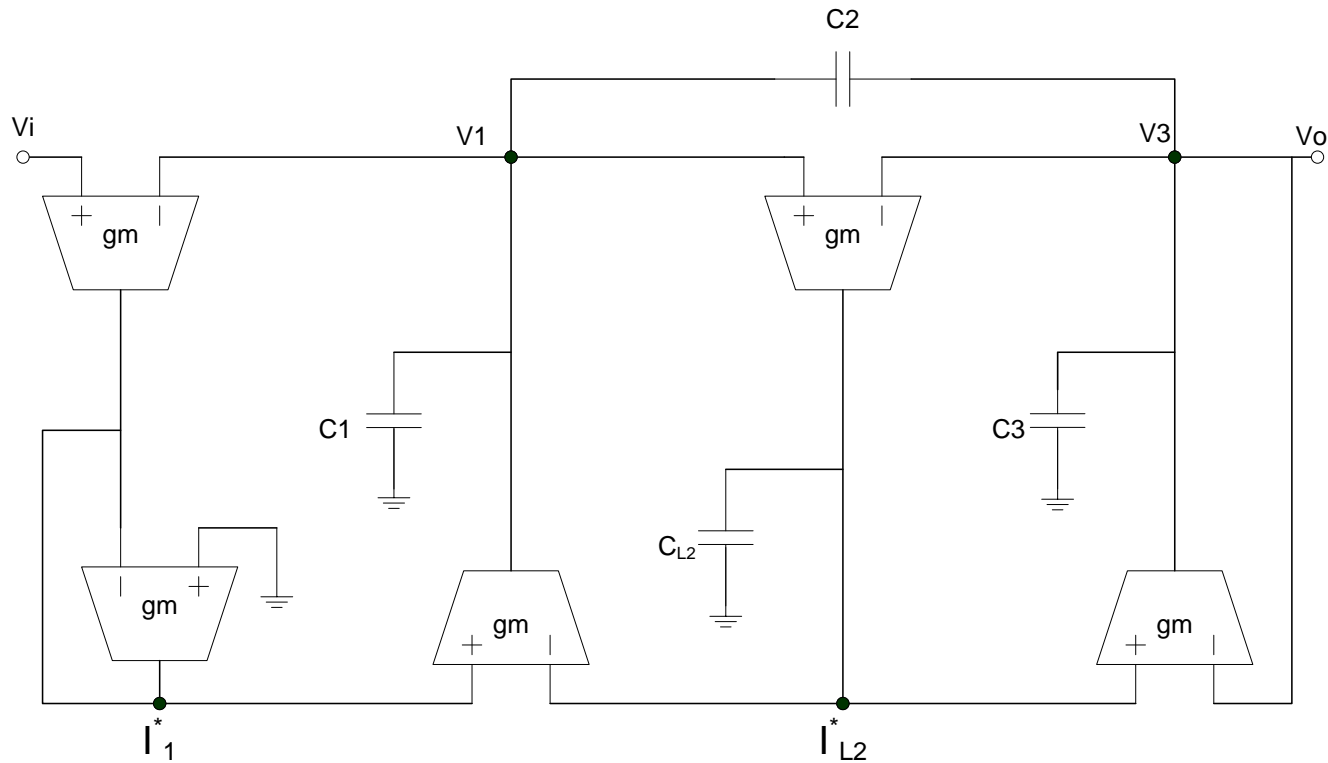

Filter Implementation: SFG

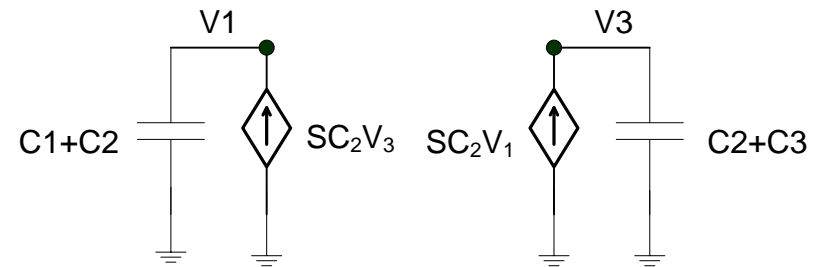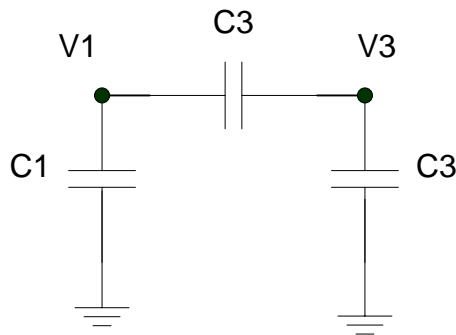Implementing transmission zeros (second approach):



$$\begin{cases} S \cdot C_1 \cdot V_1 + S \cdot C_2 (V_1 - V_3) \\ S \cdot C_3 \cdot V_3 + S \cdot C_2 (V_3 - V_1) \end{cases} \equiv \begin{cases} S \cdot (C_1 + C_2) \cdot V_1 - S \cdot C_2 V_3 \\ S \cdot (C_2 + C_3) \cdot V_3 - S \cdot C_2 V_1 \end{cases}$$



Filter Implementation: SFG

43/61


Implementing transmission zeros (second approach):

$$\left\{ \begin{array}{l} I_1^* = V_i - V_1 \\ V_1 = \frac{1}{S(C_1 + C_2) \cdot R} [I_1^* - I_{L2}^* - S \cdot C_2 \cdot R \cdot V_3] \\ = \frac{1}{S(C_1 + C_2) \cdot R} (I_1^* - I_{L2}^*) + \frac{C_2}{C_1 + C_2} \cdot V_3 \\ I_{L2}^* = \frac{R}{S \cdot L_2} (V_1 - V_3) \\ V_3 = \frac{1}{S \cdot (C_2 + C_3) \cdot R} [I_{L2}^* - I_3^* - S \cdot C_2 \cdot R \cdot V_1] \\ = \frac{1}{S(C_2 + C_3) \cdot R} (I_{L2}^* - I_3^*) + \frac{C_2}{C_2 + C_3} \cdot V_1 \\ I_3^* = V_3 \end{array} \right.$$



Filter Implementation: SFG

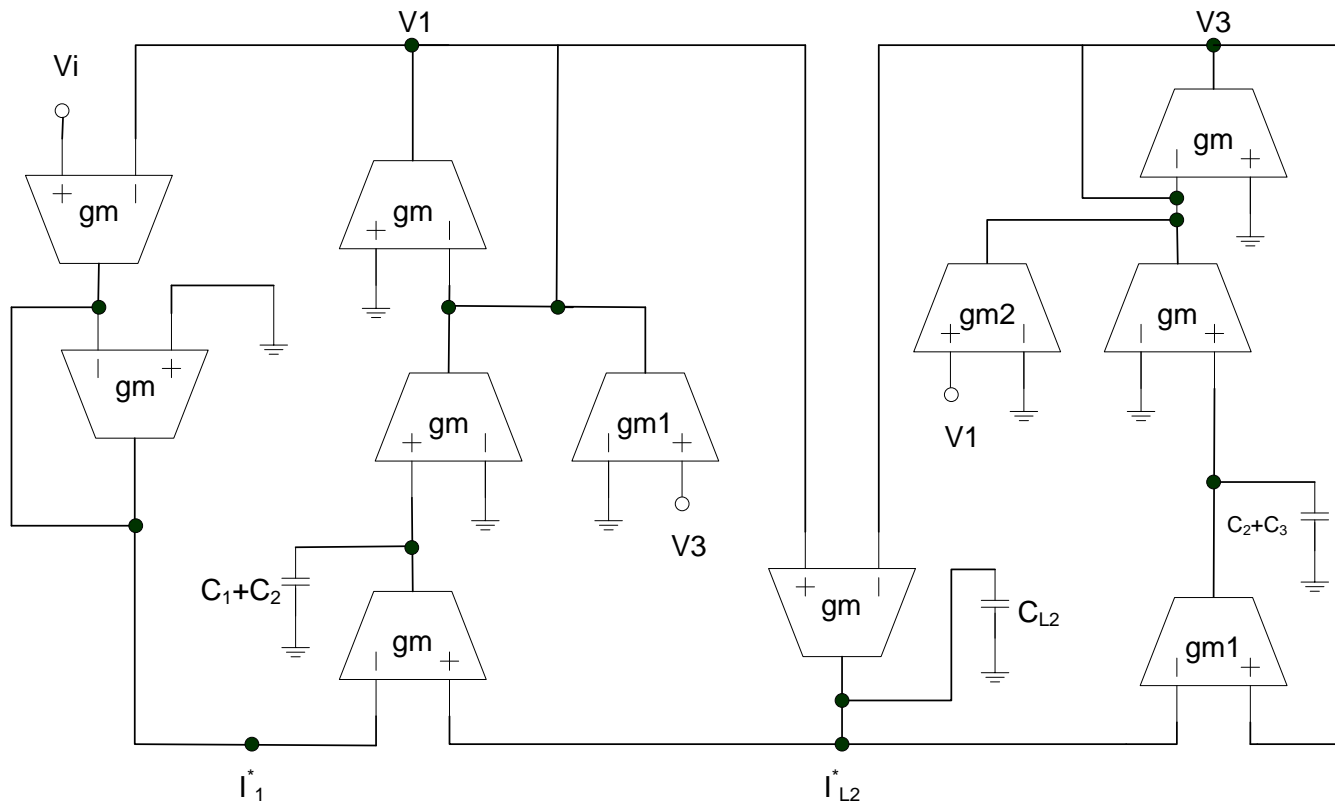Implementing transmission zeros (second approach):



Filter Implementation: Chain

45/61

Specifications

- 1- Uses a chain of first/second order filters
- 2- Each stage could be implemented based on LC ladder
- 3- High sensitivity to device variation
- 4- Low number of Gm cells
- 5- DR could be simply optimized
- 6- Tuning is much easier than Replacement technique



Filter Implementation: Chain


46/61

Two Integrator Filter Building Block (Base of many biquad stages)

$$V_{lp} = \frac{k_0 A_1 A_2}{s^2 + k_1 A_1 s + k_2 A_1 A_2}$$

$$V_{bp} = \frac{-k_0 A_1 s}{s^2 + k_1 A_1 s + k_2 A_1 A_2}$$
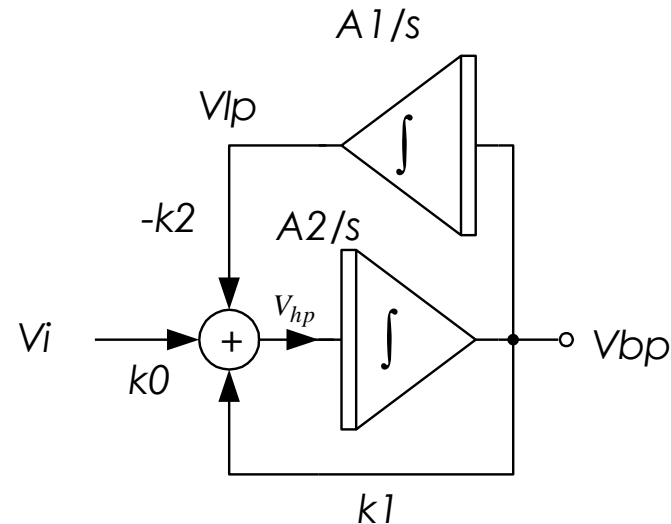
$$V_{hp} = \frac{k_0 s^2}{s^2 + k_1 A_1 s + k_2 A_1 A_2}$$




It is possible to implement all transfer functions of LP, BP, HP



Filter Implementation: Chain



Examples of Biquad Stage

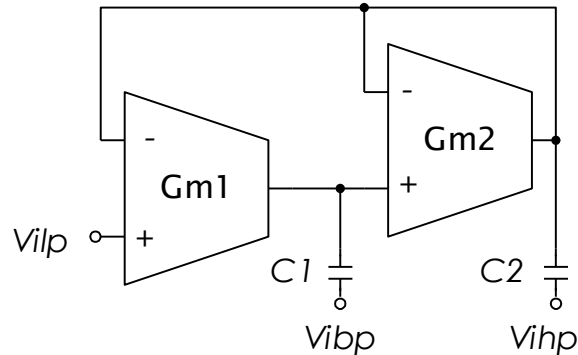

$$v_o = \frac{s^2(C_1 C_2 V_{ihp}) + s(C_1 g_{m2} V_{ibp}) + (g_{m1} g_{m2} V_{ilp})}{s^2(C_1 C_2) + s(C_1 g_{m2}) + g_{m1} g_{m2}}$$

Other possible topologies:

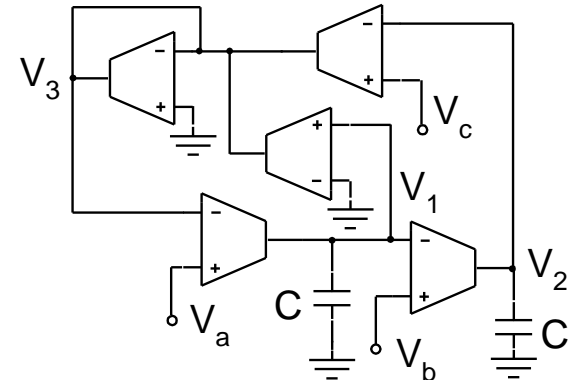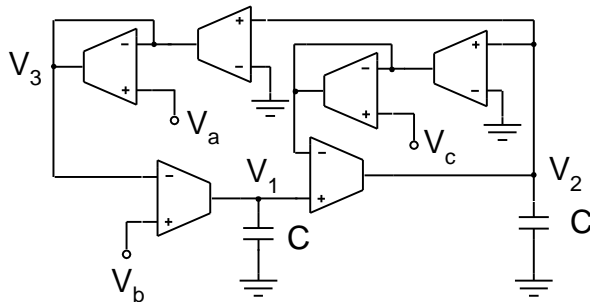Exercise: *Extract the transfer function of these biquad stages*




Filter Implementation: Chain

48/61

A complete Biquad Stage:

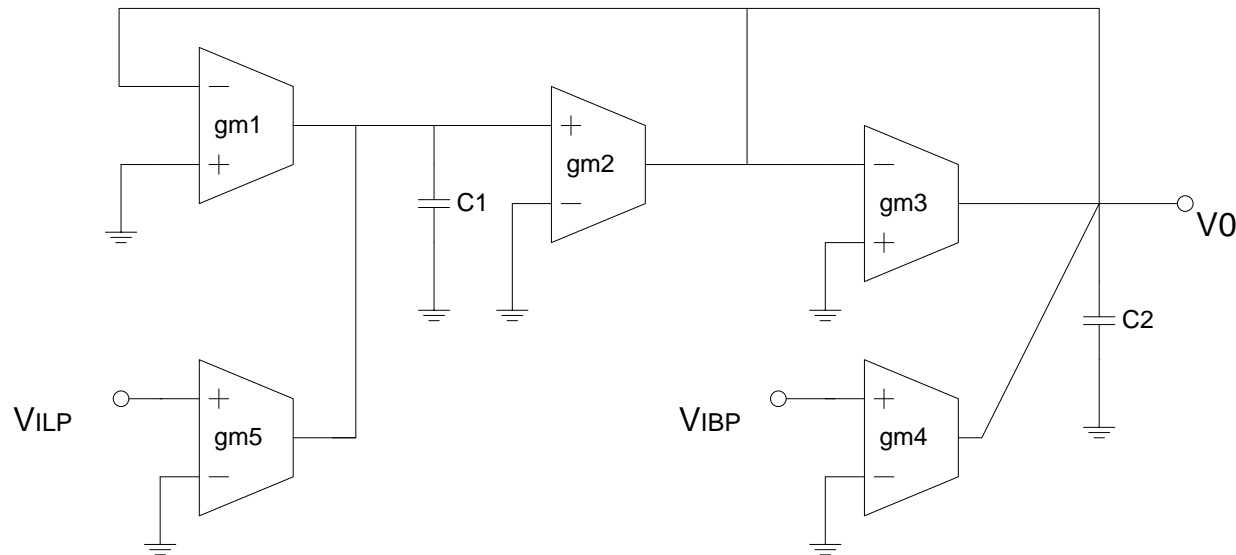
- ◆ Capability of tuning of Q or F separately for poles and zeros
- ◆ High number of G_m cells
- ◆ All nodes have capacitor, so, parasitic capacitors could be absorbed. So, no extra parasitic pole/zero will be generated and just the existing poles/zeros of filter will be changed.
- ◆ Extra G_m cells could be removed if only a LPF is required



Filter Implementation: Chain

49/61
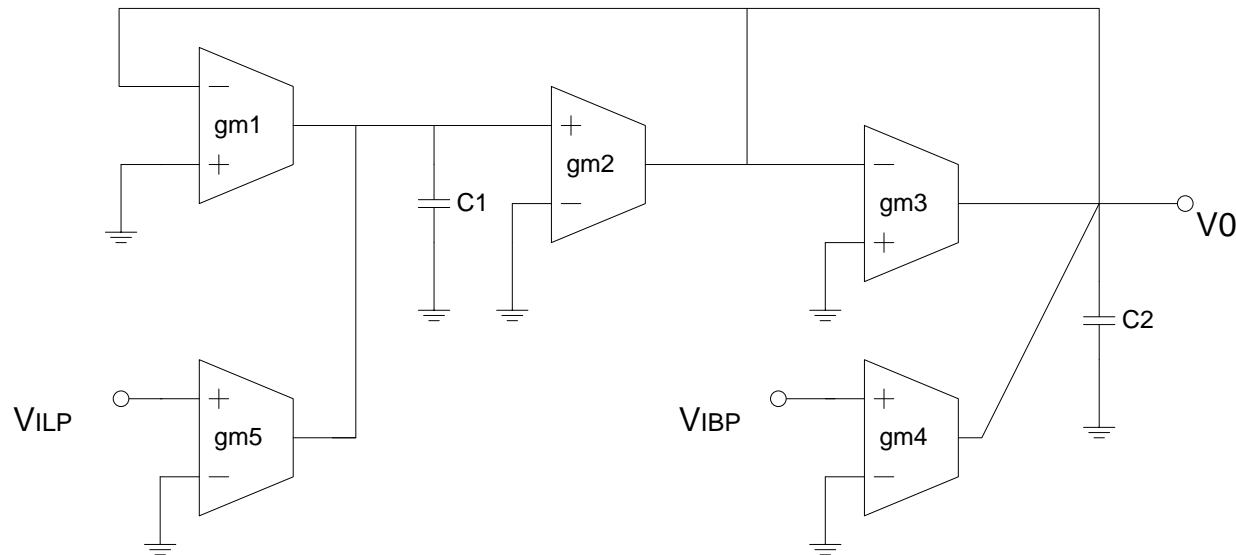
$$V_o = \frac{s^2 \cdot c_1 \cdot c_2 \cdot V_{IHP} + s \cdot c_1 \cdot gm_4 \cdot V_{IBP} + gm_2 \cdot gm_5 \cdot V_{ILP}}{s^2 \cdot c_1 \cdot c_2 + s \cdot c_1 \cdot gm_4 + gm_2 \cdot gm_1}$$



Filter Implementation: Chain


Input Condition	Transfer Function	Type of Circuit	ω_0	Q
$V_i = V_{ILP}$ $V_{IBP} = V_{IHP} = 0$	$\frac{g_{m1} \cdot g_{m2}}{s^2 \cdot c_1 \cdot c_2 + s \cdot c_1 \cdot g_{m2} + g_{m1} \cdot g_{m2}}$	LP with Tunable ω_0	$\frac{gm}{\sqrt{c_1 \cdot c_2}}$	$\sqrt{\frac{c_2}{c_1}}$
$V_i = V_{IBP}$ $V_{ILP} = V_{IHP} = 0$	$\frac{s \cdot c_1 \cdot g_{m2}}{s^2 \cdot c_1 \cdot c_2 + s \cdot c_1 \cdot g_{m2} + g_{m1} \cdot g_{m2}}$	BP with Tunable ω_0	$\frac{gm}{\sqrt{c_1 \cdot c_2}}$	$\sqrt{\frac{c_2}{c_1}}$
$V_i = V_{IHP}$ $V_{ILP} = V_{IBP} = 0$	$\frac{s^2 \cdot c_1 \cdot c_2}{s^2 \cdot c_1 \cdot c_2 + s \cdot c_1 \cdot g_{m2} + g_{m1} \cdot g_{m2}}$	HP with Tunable ω_0	$\frac{gm}{\sqrt{c_1 \cdot c_2}}$	$\sqrt{\frac{c_2}{c_1}}$
$V_i = V_{ILP} = V_{IHP}$ $V_{IBP} = 0$	$\frac{s^2 \cdot c_1 \cdot c_2 + g_{m1} \cdot g_{m2}}{s^2 \cdot c_1 \cdot c_2 + s \cdot c_1 \cdot g_{m2} + g_{m1} \cdot g_{m2}}$	Notch with Tunable ω_0	$\frac{gm}{\sqrt{c_1 \cdot c_2}}$	$\sqrt{\frac{c_2}{c_1}}$



Filter Implementation: Chain

51/61

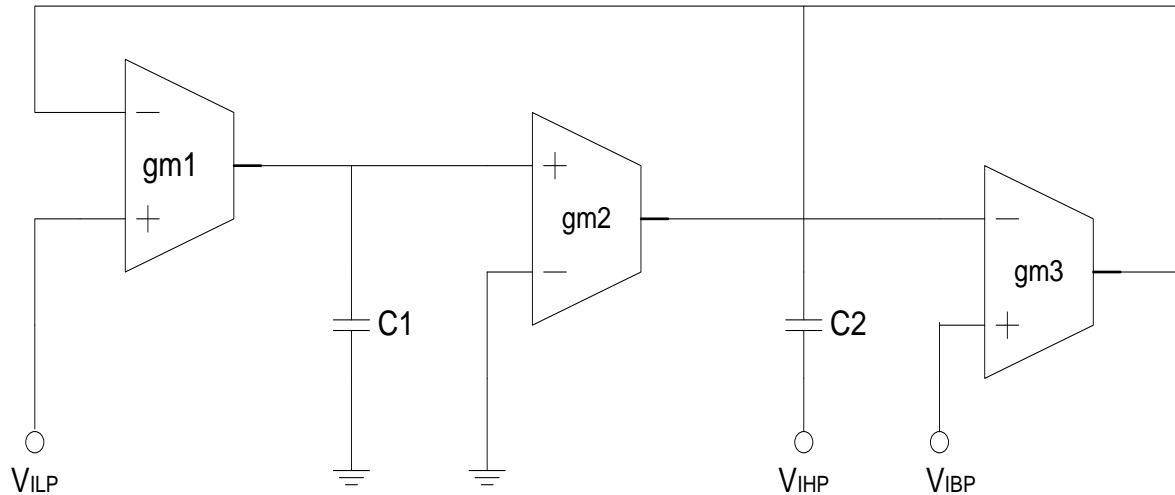Equivalent Biquad stage uses two-input Gm cells



Filter Implementation: Chain

52/61

Example 1: Lowpass Biquad stage

KCLs


$$S \cdot V_{BP} \cdot C_1 = gm_1 \cdot V_i - gm_2 \cdot V_{BP} - gm_4 \cdot V_{LP}$$

$$S \cdot V_{LP} \cdot C_2 = gm_3 \cdot V_{BP}$$

⇒

$$\frac{V_{BP}}{V_i} = \frac{S \cdot \frac{gm_1}{C_1}}{S^2 + S \cdot \frac{gm_2}{C_1} + \frac{gm_3 \cdot gm_4}{C_1 \cdot C_2}} = \frac{S \cdot \frac{gm_1}{C_1}}{S^2 + \frac{\omega_0}{Q} \cdot S + \omega_0^2}$$

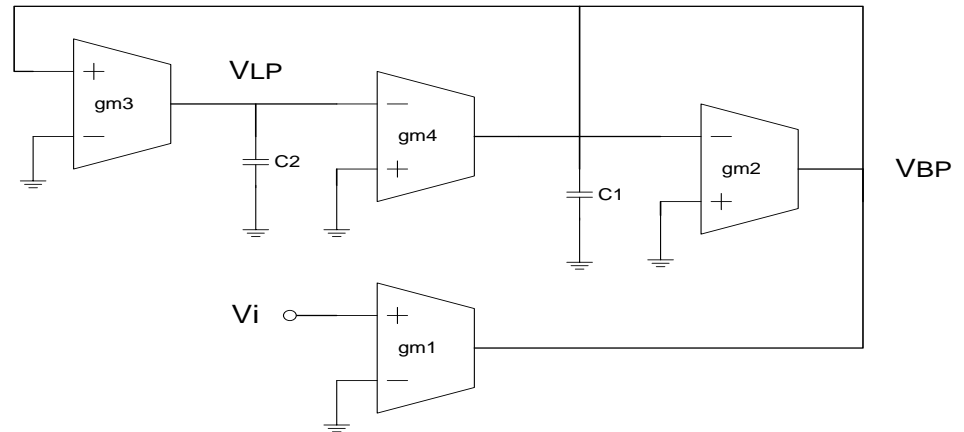
$$\frac{V_{LP}}{V_i} = \frac{\frac{gm_3 \cdot gm_4}{C_1 \cdot C_2}}{S^2 + S \cdot \frac{gm_2}{C_1} + \frac{gm_3 \cdot gm_4}{C_1 \cdot C_2}}$$



Filter Implementation: Chain

53/61

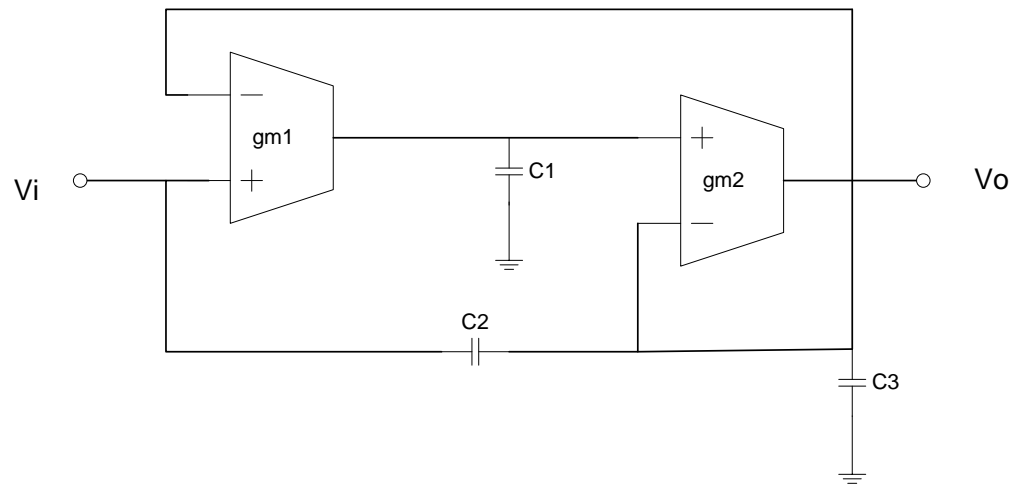Example 2: Find the transfer function of this circuit




$$\frac{V_o}{V_i} = \frac{C_2}{C_1 + C_2} \cdot \frac{S^2 + \frac{gm_1 \cdot gm_2}{C_1 \cdot C_2}}{S^2 + S \cdot \frac{gm_2}{C_1 + C_2} + \frac{gm_1 \cdot gm_2}{C_1 \cdot (C_2 + C_3)}}$$



Filter Implementation: Chain

54/61

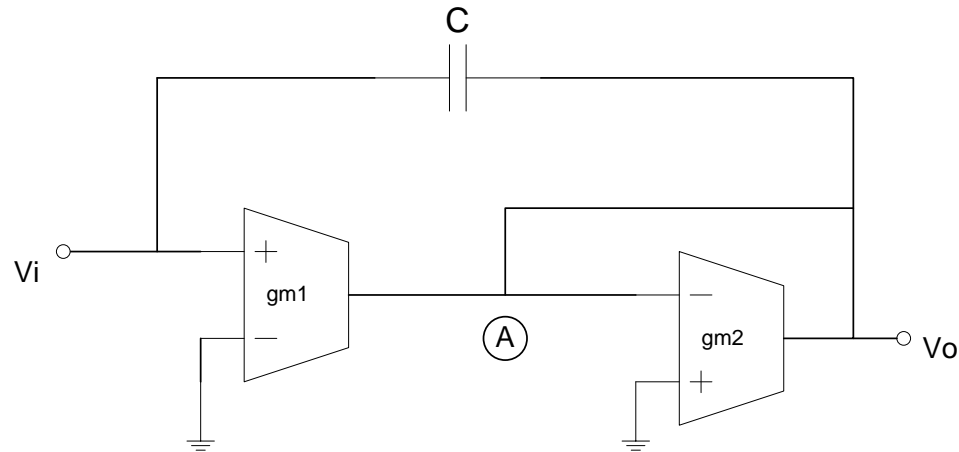Example 3: Find the transfer function of this circuit



KCL @ node A →

$$gm_1 \cdot V_i - gm_2 \cdot V_o + S \cdot C(V_i - V_o) = 0$$

$$V_i (gm_1 + S \cdot C) = V_o (gm_2 + S \cdot C)$$

⇒

$$\frac{V_o}{V_i} = \frac{gm_1 + S \cdot C}{gm_2 + S \cdot C}$$



Main characteristics of Biquad Stage

- 1- Nodes without Capacitor leads to high sensitivity to stray caps
- 2- Independent DR optimization of overall filter and biquad stage
- 3- Independent Freq and Q tuning capability
- 4- Q depends on ratio of capacitors and transconductors, so it could be accurate
- 5- Parasitic capacitors at the input or output of Gm cell, will not create new parasitic poles/zeros




Two Input Gm Cells

56/61

Using Two Input Gm Cells for Simplifying the Implementation:

Two Input Gm Cell

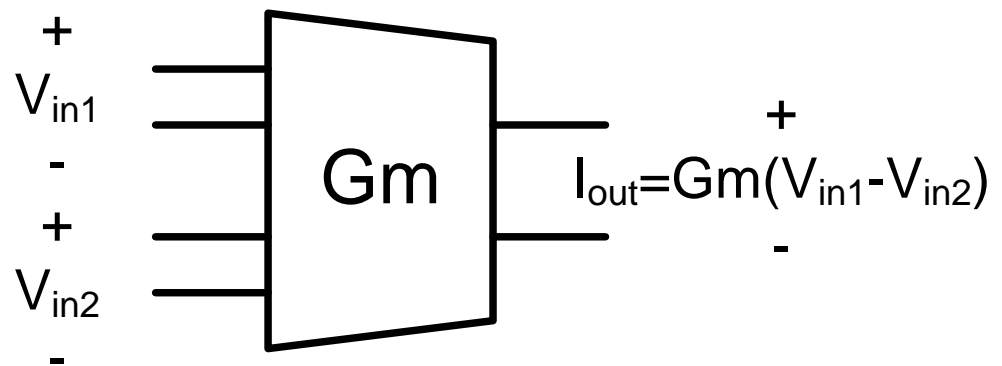
- ◆ Reduces the circuit complexity
- ◆ Saves the number of output stages
- ◆ Saves the number of required CMFB circuits



Two Input Gm Cells

57/61


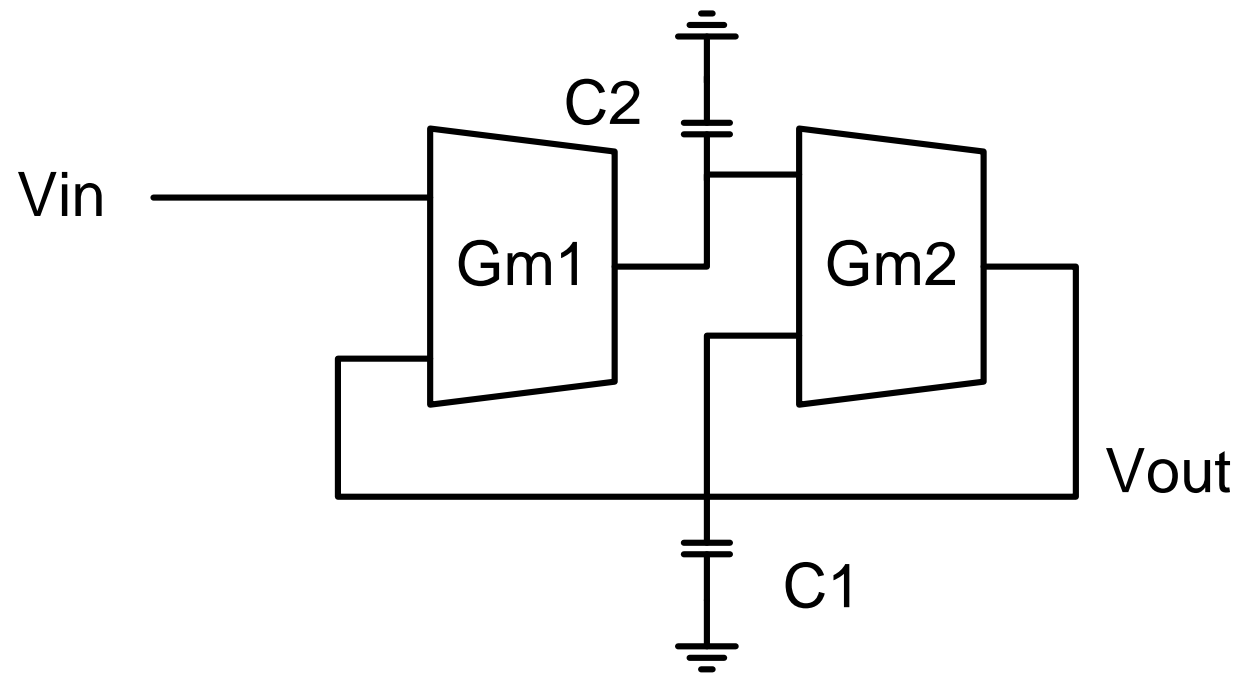
Example: Implementing Biquad Filter by two input Gm cells



Two Input Gm Cells

Filter implementation using two input Gm cells

[JSSC, 1998, Yoo]

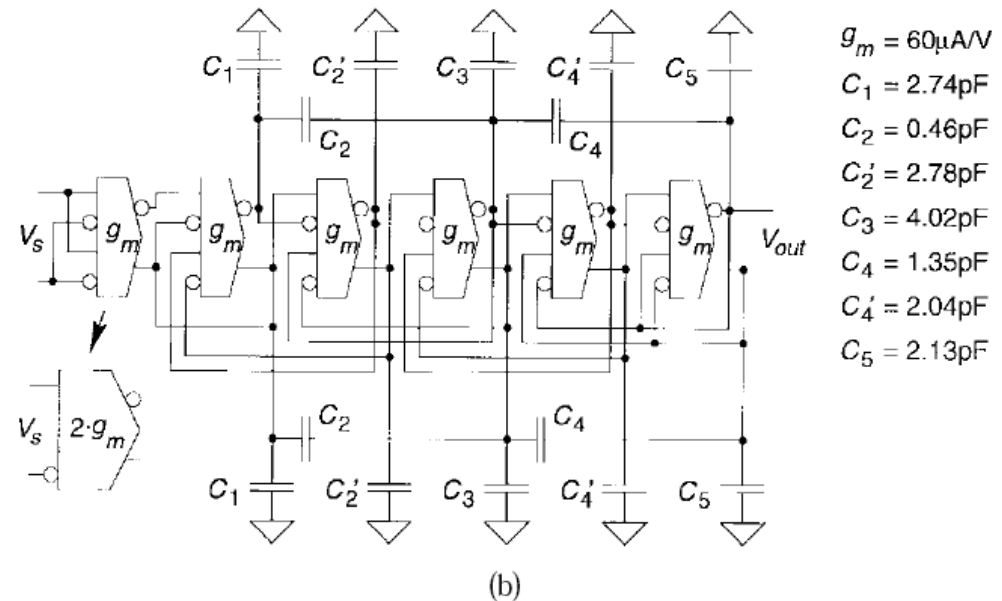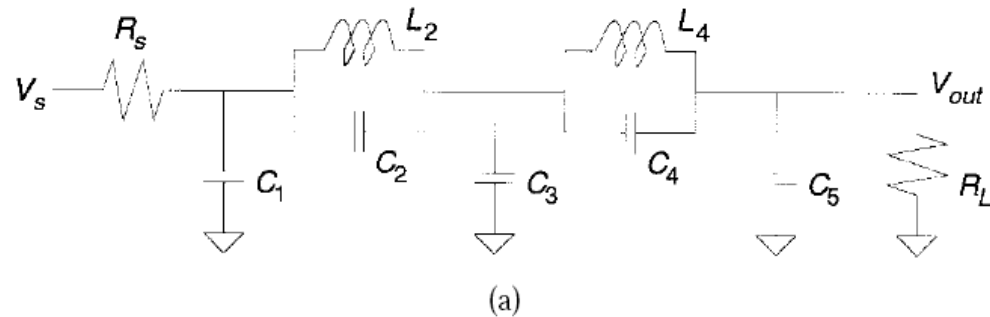

Single / Differential Ended

61/61

Converting S to D:

Advantages:

- Less sensitivity to supply/substrate noise
- Linearity (better HD2)
- Higher DR

