

# ANALOG CMOS INTEGRATED CIRCUIT DESIGN

PROJECT پروژه درس (۴ نمره)  
طراحی و مشخصه یابی یک تقویت کننده عملیاتی

---

Hossein Karimiyan

Department of Electrical and Computer Engineering


University of Kashan

[hkarimiyan@kashanu.ac.ir](mailto:hkarimiyan@kashanu.ac.ir)


Tel: 5591-3475
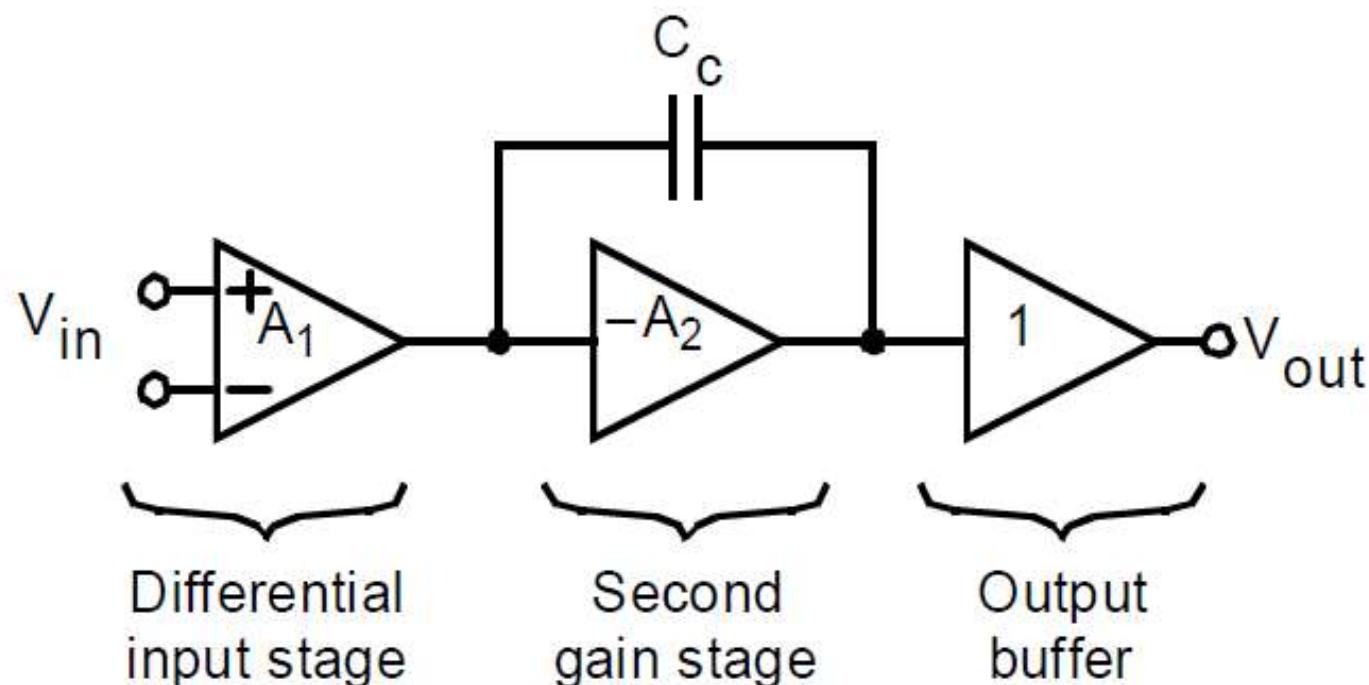
# CMOS Opamp


- Output buffer is typically used to drive resistive loads
- For capacitive loads (typical case in CMOS) buffer is not required.




# Simple One-Stage OPAMP

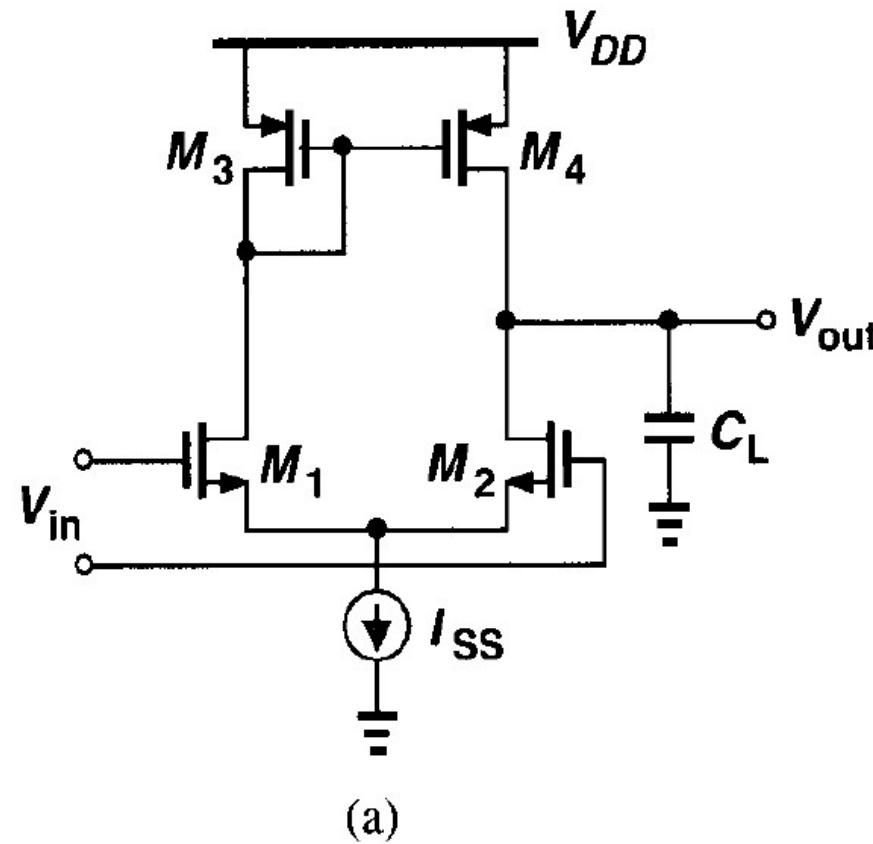

# Gain Boosting

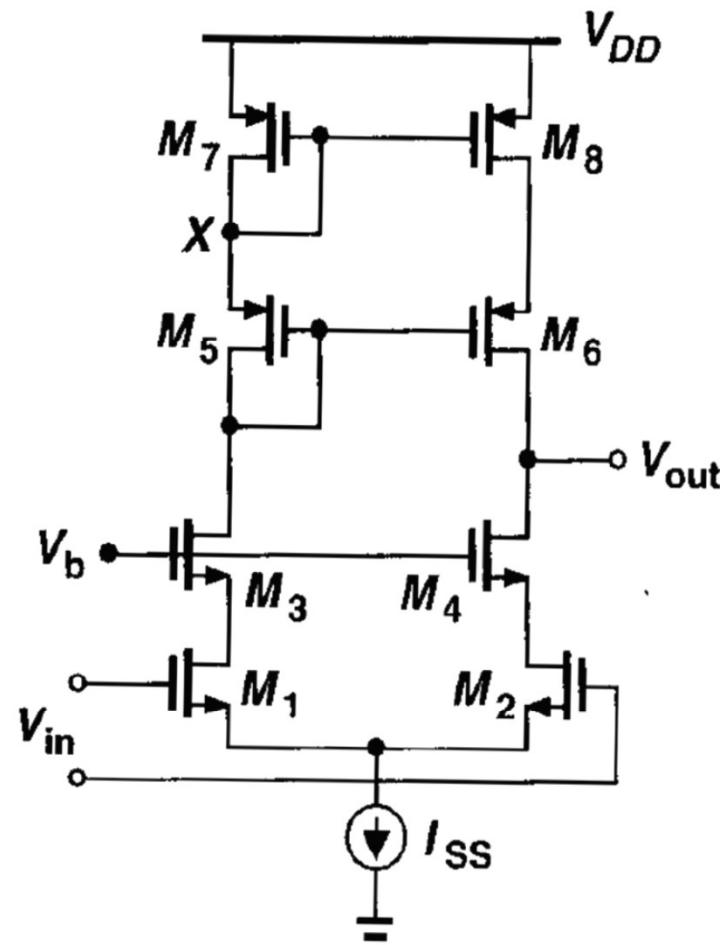


(a)

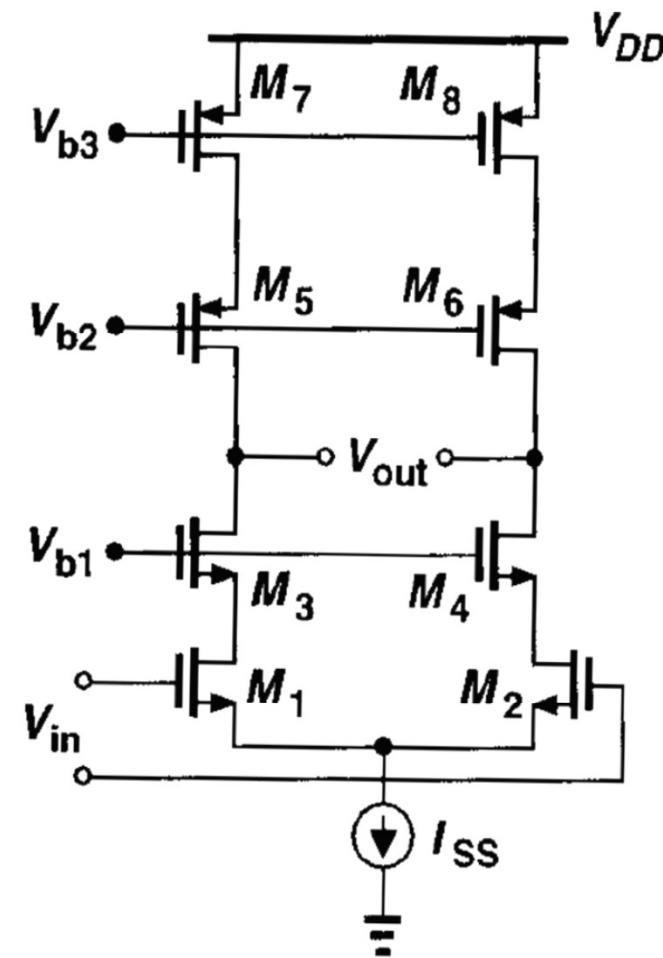

(b)

# Two Stage Op Amp

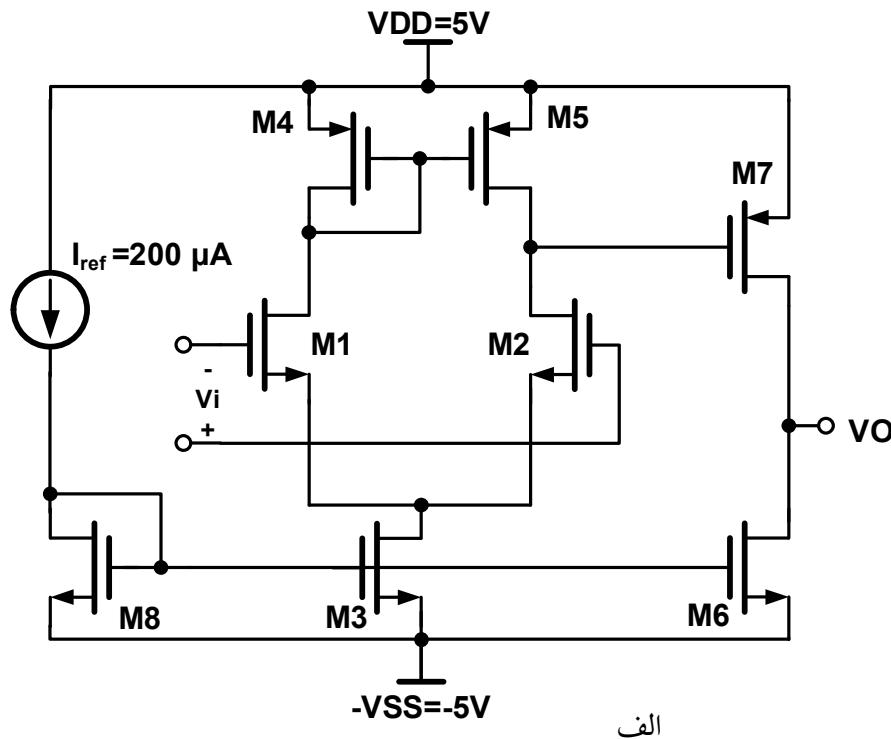


For M1-8 :  $|V_t| = 1V$ ,  $|V_A| = 25V$   
 $\mu_n C_{ox} = 20 \mu\text{A/V}^2$ ,  $\mu_p C_{ox} = 10 \mu\text{A/V}^2$


M8	M7	M6	M5	M4	M3	M2	M1	W/L
10	20	10	20	20	15	10	10	W/L
								$I_D(\mu\text{A})$
								$ V_{GS} (\text{V})$
								$g_m(\mu\text{A/V})$
								$r_o(\text{M}\Omega)$

بـ

# Unity Gain Configuration

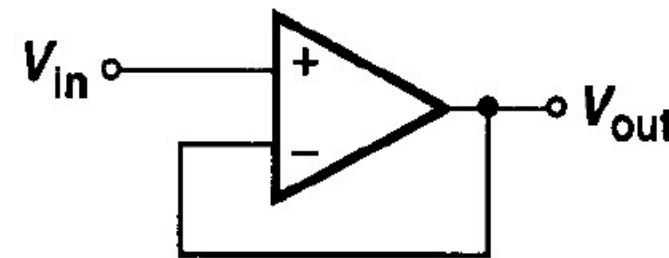

# Gain

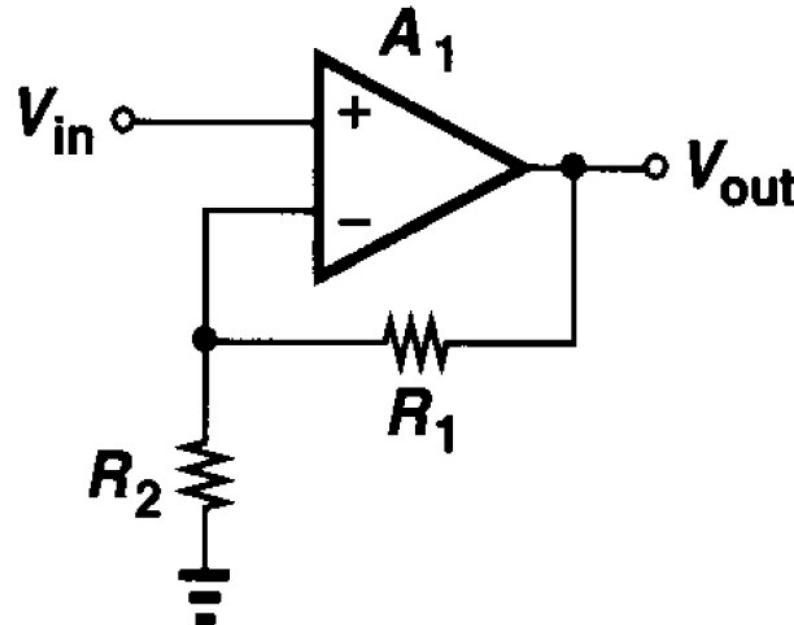

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1} \\ &= \frac{R_1 + R_2}{R_2} \frac{A_1}{\frac{R_1 + R_2}{R_2} + A_1}.\end{aligned}$$

$$\frac{V_{out}}{V_{in}} \approx \left(1 + \frac{R_1}{R_2}\right) \left(1 - \frac{R_1 + R_2}{R_2} \frac{1}{A_1}\right)$$

# مشخصات مطلوب

- Technology: 180nm
- Open loop gain, minimum: 1000
- Internal Freq. compensation,
- Minimum 10 MHz bandwidth
- Low-power dissipation
- Maximum output swing
- Unity gain stability

# تحویل پروژه طراحی

- تاریخ تحویل: آخر وقت 25 اسفند 1401
- خروجیهای لازم که باید تحویل شوند:
  - گزارش طراحی
  - اندازه تمام المانها
  - نتایج شبیه سازی صحت کار تک تک بخشها
  - نتایج شبیه سازی کل مدار در حالت حلقه باز و حلقه بسته
  - پاسخ فرکانسی تک تک بخشهای مدار
  - پاسخ فرکانسی کل مدار
- گزارش چیدمان فیزیکی المانها و طرح Layout (نمره اضافی)